

國立臺灣科技大學103學年度碩士班招生試題

系所組別：電機工程系碩士班丁二組

科目：控制系統與數位邏輯

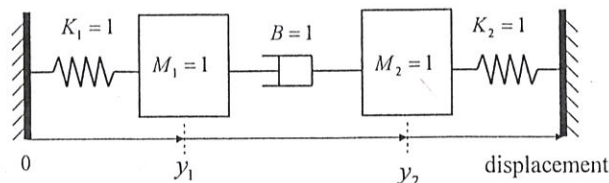
(總分為100分)

Problem 1: (15 points)


$$\text{Let signals } x(t) = \begin{cases} \sin t & 0 \leq t \leq \pi \\ 0 & \text{otherwise} \end{cases} \text{ and } h(t) = \begin{cases} \cos t & 0 \leq t \leq \pi \\ 0 & \text{otherwise} \end{cases}$$

(a) compute the convolution signal $y(t) = x(t) * h(t) = \int_{-\infty}^{\infty} x(\tau)h(t-\tau)d\tau, -\infty < t < \infty$.

(10 points)

(b) Plot the signal $y(t), -\infty < t < \infty$. (5 points)**Problem 2: (15 points)**Given the mass-spring-damper mechanical system as shown below, in which y_1 and y_2 are the displacement of mass 1 and mass 2, respectively;(a) find out the state-space representation of the system $\dot{x} = Ax$, where the statevariables $x = [x_1 \ x_2 \ x_3 \ x_4]^T = [y_1 \ y_2 \ \dot{y}_1 \ \dot{y}_2]^T$. (10 points)

(b) Determine whether the system is asymptotically stable, marginally stable or unstable, why and why not? (5 points)

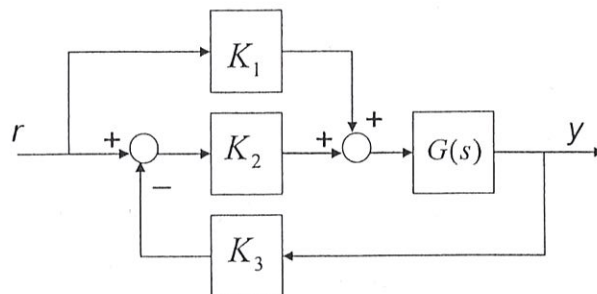Problem 3: (20 points)Consider the following feedback control system, where $G(s) = \frac{s}{s^2 + 4}$,(a) draw the root locus of the system for $0 \leq K_1 < \infty$ and $K_2 = K_3 = 1$. (5 points)(b) Draw the root locus of the system for $0 \leq K_2 < \infty$ and $K_1 = K_3 = 1$. (5 points)(c) Plot the curve of phase margin v.s. $K_3, 0 < K_3 < \infty$ and $K_1 = K_2 = 1$. (5 points)(d) What are the differences of the roles of K_1, K_2 and K_3 in system transfer functions and stability? (5 points)

國立臺灣科技大學103學年度碩士班招生試題

系所組別：電機工程系碩士班丁二組

科目：控制系統與數位邏輯

(總分為100分)

Problem 4: (10 points)Implement $F = wx' + y'z' + w'yz'$ with two-level NOR gate circuit.**Problem 5: (20 points)**

A sequential circuit with two D flip-flops A and B , two inputs x and y , and one output z is specified by the following next-state equations: $A(t+1) = x'y + xB$,

 $B(t+1) = x'A + xB$, and output equation: $z = A$.

- (a) Draw the logic diagram of the circuit (6 points).
- (b) List state table for this sequential circuit (7 points).
- (c) Draw the corresponding state diagram (7 points).

Problem 6: (20 points)

Design a counter with T-flip-flops that goes through the following binary repeated sequence: 0, 1, 3, 7, 6, 4. Show that when binary states 010 and 101 are taken to be don't-care conditions, the counter may not operate properly. Find a way to correct the design.

