

國立臺灣科技大學 107 學年度碩士班招生試題

系所組別：電機工程系碩士班甲組

科目：電力系統

(總分為 100 分)

- Three loads are connected in parallel across a 11.8 kV three-phase supply.
  - Load 1: Inductive load, 110 kW and 630 kVar.
  - Load 2: Capacitive load, 200 kW at 0.8 power factor.
  - Load 3: Resistive load of 50 kW.
  - Find the total complex power, power factor, and the supply current. (6%)
  - A Y-connected capacitor bank is connected in parallel with the loads. Find the total kVar and the capacitance per phase in  $\mu F$  to improve the overall power factor to 0.8 lagging. What is the new line current? (9%)
- A three-phase, 60-Hz, untransposed transmission line runs in parallel with a telephone line for 20 km. The power line carries a balanced three-phase rms current of  $I_a = 240\angle 0^\circ$  A,  $I_b = 240\angle -120^\circ$  A and  $I_c = 240\angle -240^\circ$  A. The line configuration is as shown in Figure 1 where the d and e are the pair of telephone line. Assume zero current flows in the ungrounded telephone wires. Find the magnitude of the voltage induced in the telephone line. (10%)


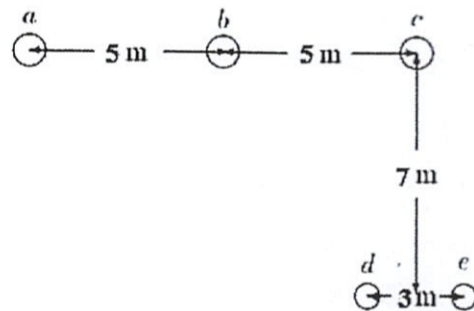


Figure 1

- A 60-kVA, 4800/2400-V single-phase transformer gave the following test results:
  - Rated voltage is applied to the low voltage winding and the high voltage winding is open-circuited. Under this condition, the current into the low voltage winding is 2.2A and the power taken from the 2400V source is 3500W.
  - A reduced voltage of 1250V is applied to the high voltage winding and the low voltage winding is short-circuited. Under this condition, the current flowing into the high voltage winding is 12.5A and the power taken from the 1250V source is 4200W.
  - Determine parameters of the equivalent circuit referred to the high voltage side. (12%)
  - Determine voltage regulation and efficiency when transformer is operating at full-load, 0.8 power factor lagging, and a terminal voltage of 2400V. (6%)
  - What is the load kVA for maximum efficiency and the maximum efficiency at 0.8 power factor? (4%)
  - Determine the efficiency when transformer is operating at half load, 0.6 power factor lagging, and a terminal voltage of 2400V. (3%)

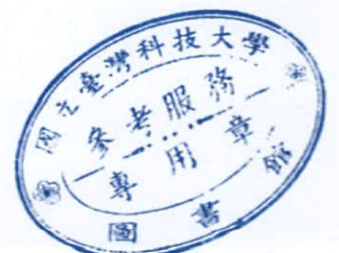

國立臺灣科技大學 107 學年度碩士班招生試題

系所組別：電機工程系碩士班甲組

科目：電力系統

(總分為 100 分)

4. The sending-end and receiving-end voltages of a transmission line at a 100 MW load are equal at 115 kV. The per-phase line impedance is  $4+j7 \Omega$ . Calculate the maximum steady-state power that can be transmitted over the line. (15%)
5. An interconnected generator-reactor system is shown in Figure 2. The base values for the given percent reactances are the ratings of the individual pieces of equipment. A three-phase short-circuit occurs at point F. Determine the fault current if the busbar line-to-line voltage is 11 kV. (15%)

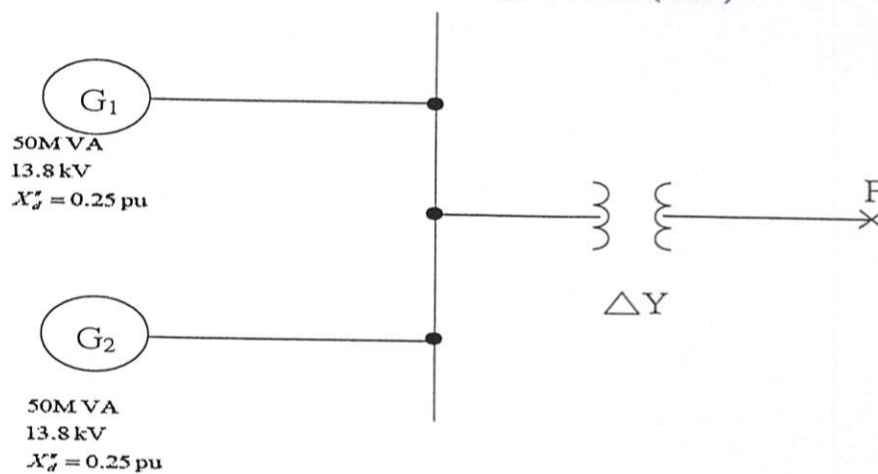


Figure 2

6. Consider a system without generator limits (see Figure 3). Assume that

$$\text{The incremental cost for } P_{G1}: IC_1 = 0.006P_{G1} + 3.8 \text{ \$/MWh}$$

$$\text{The incremental cost for } P_{G2}: IC_2 = 0.007P_{G2} + 4.1 \text{ \$/MWh}$$

$$\text{The total line loss: } P_L = 0.001(P_{G2} - 50)^2 \text{ MW}$$

Find the optimal generation for each plant and the power loss in the transmission link. [Hint: If the initial value for  $P_{G1}$  is set to 200 MW, only a few iterations are required for convergence.] (20%)

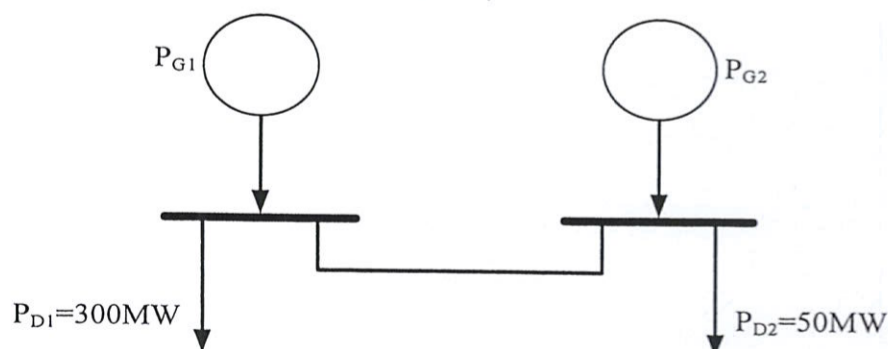


Figure 3

