


國立臺灣科技大學 107 學年度碩士班招生試題

系所組別：電機工程系碩士班丁二組


科目：控制系統與數位邏輯

Problem 1: (15 points) 說明：計算題 15 分

Consider the following system block diagram (SBD), use only three basic SBD operators:

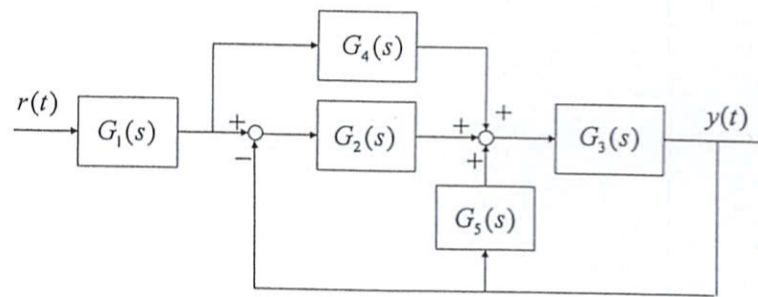 series(G_1, G_2) $\equiv G_1 G_2$, parallel(G_1, G_2) $\equiv G_1 + G_2$, and feedback($G_1, \pm G_2$) $\equiv \frac{G_1}{1 \mp G_1 G_2}$, to find thesystem transform function $G(s) = \frac{Y(s)}{R(s)}$. There is no point if you use other methods to solve this problem.**Problem 2: (15 points) 說明：計算題 15 分**

Draw the Bode plot of a negative unity-feedback system with loop transfer function

$$L(s) = \frac{10(s+10)}{s(s+1)(s+100)}$$
 , and estimate the gain margin (GM) and phase margin (PM) from your Bode plot as accuracy as possible.
Problem 3: (15 points) 說明：計算題 15 分Draw the root-locus plot (i.e. close-loop poles v.s. K) of a negative unity-feedback system
 with loop transfer function $L(s) = \frac{11s+6}{s(s+6)(s+K)}$, $K > 0$, and determine the value of K such that the close-loop system has a pole at $s = -0.5$.
Problem 4: (5 points) 說明：設計題 5 分Write an algorithm to implement a PI controller $\frac{U(s)}{E(s)} = P + \frac{I}{s}$, $P, I > 0$, the input is the systemerror $e[n] = r[n] - y[n]$ and the output is the control input $u[n]$, where discrete-time signals $e[n] = e(nT)$, $r[n] = r(nT)$, $y[n] = y(nT)$ and $u[n] = u(nT)$, $n = 0, 1, 2, \dots$, and T is the sampling time.

國立臺灣科技大學 107 學年度碩士班招生試題

系所組別：電機工程系碩士班丁二組

科 目：控制系統與數位邏輯

Problem 5: The four-bit universal shift register is shown in Fig. 1. Draw a block diagram of the IC with 16 pins, showing all inputs, outputs and two pins for the power supply. In addition, a function table for this IC is depicted. (12 points)


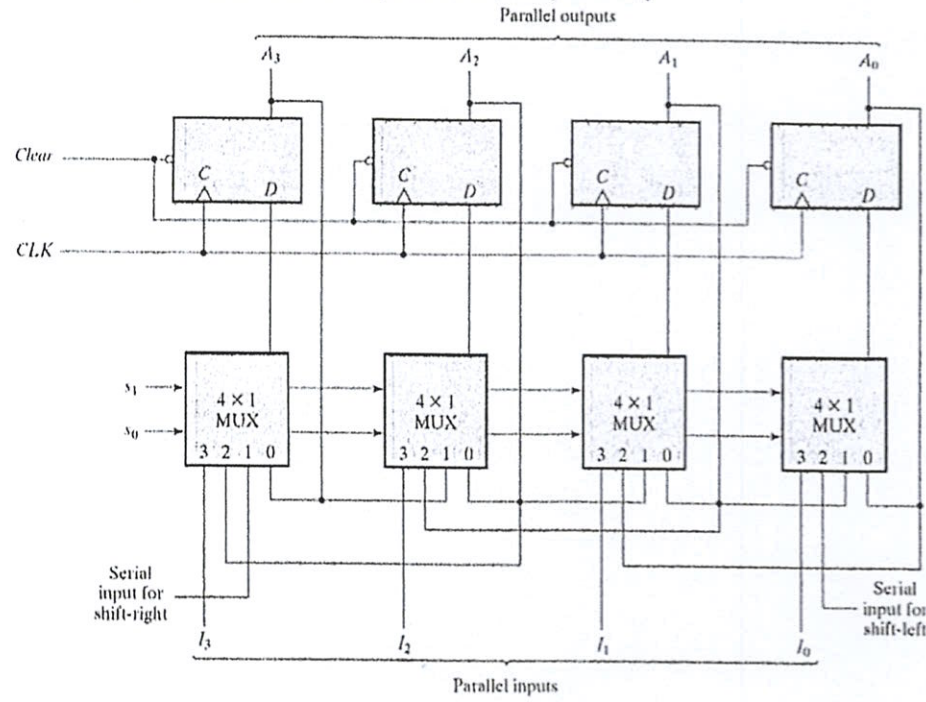


Fig. 1. Four-bit universal shift register.

Problem 6: Design a three-bit counter using T-FF such that the operation $000 \rightarrow 111 \rightarrow 110 \rightarrow 101 \rightarrow 100 \rightarrow 011 \rightarrow 010 \rightarrow 001 \rightarrow 000$. The results must include state table, K-map, and logic diagram. (18 points)

 Problem 7: Consider the 4-bit binary counter in Fig. 2. Given the following signals: (i) **initial begin** $CLK=0$; #5 forever $CLK=\sim CLK$; **end.** (ii) **initial fork** $Clear_b=0$; #20 $Clear_b=1$; **join.** (iii) **initial fork** $Count=0$; #50 $Count=1$; #150 $Count=0$; #200 $Count=1$; **join.** (iv) **initial fork** $Load=0$; #250 $Load=1$; #260 $Load=0$; **join.** Plot and explain the responses including, CLK , $Clear_b$, $Count$, $Load$, $\{I_0, I_1, I_2, I_3\}$, $\{A_0, A_1, A_2, A_3\}$, and C_out for total 350ns. (20 points)



Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

(b)

Fig. 2. Four-bit binary counter.

