

國立臺灣科技大學 109 學年度碩士班招生試題

系所組別：電機工程系碩士班甲組  
 科 目：電力系統

(總分為 100 分)

1. For the three-bus system with two generators in Fig. 1, please perform one iteration of Newton's power flow method to determine voltages at bus 2 and 3. Assume that the bus 1 is the slack bus. The initial voltage at load buses are assumed to be  $1.0 \angle 0^\circ$  per unit. Note that you can use fast decoupled power flow method to simplify the Jacobian matrix. (20%)

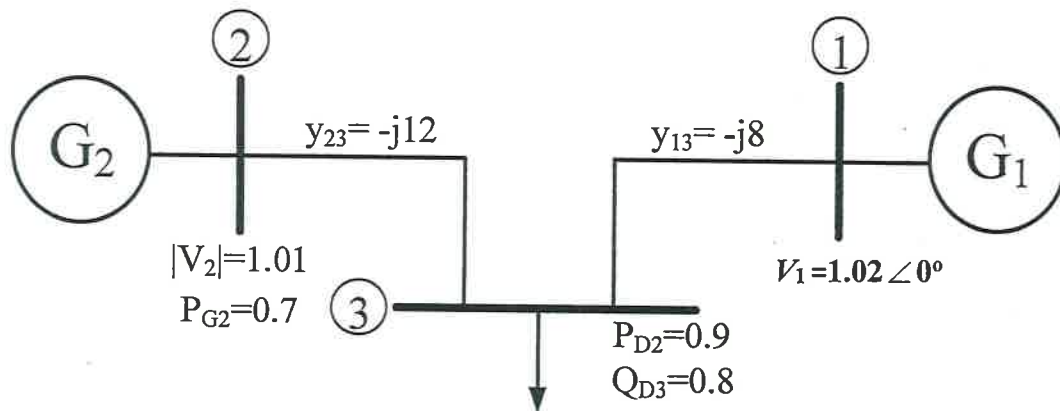


Fig. 1 Power system diagram for Q1

2. A single-phase two-conductor line is as shown in Fig. 2. Please find the inductances  $L_x$  and  $L_y$ , respectively. (15%)

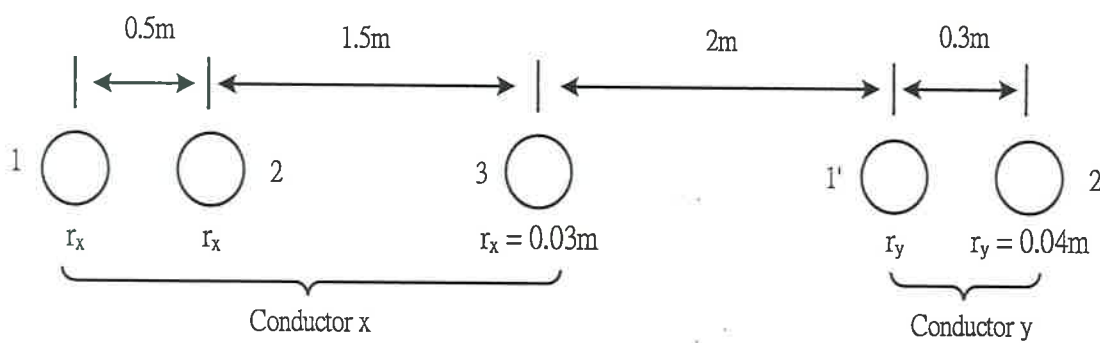


Fig. 2 The configuration of the single-phase two-conductor line for Q2

3. A three-phase, 60 Hz, 345 kV, 200 km has the following line constants:

$$z = 0.032 + j 0.35 \Omega/\text{km}$$

$$y = j 4.2 \times 10^{-6} \text{ S}/\text{km}.$$

Full load at the receiving end of the line is 700 MW at 0.99 power factor leading and at 95% of rated voltage. Please determine the voltage regulation of the line. (15%)



## 國立臺灣科技大學 109 學年度碩士班招生試題

系所組別：電機工程系碩士班甲組

科目：電力系統

(總分為 100 分)

4. The one-line diagram of a simple power system is shown in Fig. 3. The ratings and reactances of the generators and transformers are

$$G_1 \text{ and } G_2: 100 \text{ MVA, } 20\text{kV} \quad X''_d = X_1 = X_2 = 12\%, \quad X_0 = 6\%, \quad X_n = 4\%$$

$$T_1 \text{ and } T_2: 100 \text{ MVA, } 20/220\text{kV} \quad X = 8\%$$

Both transformers are solidly grounded on one side in the figure. On a chosen base of 100MVA, 220kV in the transmission line circuit, the line reactances of  $L_{12}$  are  $X_1 = X_2 = 13\%$  and  $X_0 = 25\%$ . The line reactances of  $L_{13}$  are  $X_1 = X_2 = 13\%$  and  $X_0 = 32\%$ . The line reactances of  $L_{23}$  are  $X_1 = X_2 = 20\%$  and  $X_0 = 70\%$ . The system is operating at nominal voltage without pre-fault currents.

Determine the fault current for the following faults.

(a) A single line-to-ground fault at bus 2 through a fault impedance  $Z_f = j0.05$  per unit. (10%)

(b) A line-to-line fault at bus 3 through a fault impedance  $Z_f = j0.1$  per unit. (15%)

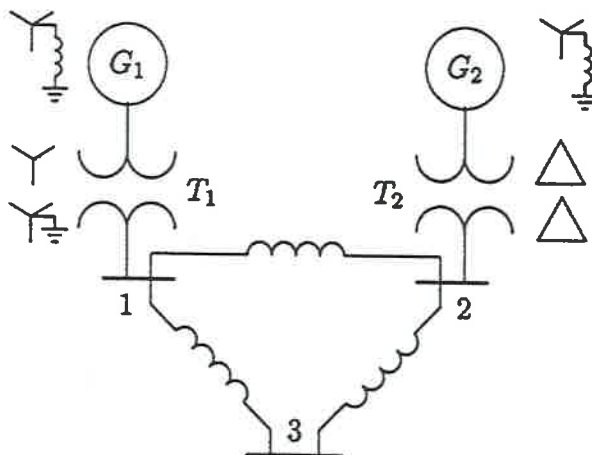


Fig. 3. The one-line diagram for Q4



## 國立臺灣科技大學 109 學年度碩士班招生試題

系所組別：電機工程系碩士班甲組

科 目：電力系統

(總分為 100 分)

5. In a three-bus system, three generating units are connected at buses 1, 2 and 3 and have the fuel-cost in \$/h given in the following equations.

$$f_1(P_{g1}) = 0.004P_{g1}^2 + 7.5 P_{g1} + 350 \quad (\$/h)$$

$$f_2(P_{g2}) = 0.008P_{g2}^2 + 7.3 P_{g2} + 550 \quad (\$/h)$$

$$f_3(P_{g3}) = 0.007P_{g3}^2 + 6.4 P_{g3} + 450 \quad (\$/h)$$

where  $P_{g1}$ ,  $P_{g2}$  and  $P_{g3}$  are in MW. Plant outputs are subject to the following limits

$$10 \text{ MW} \leq P_{g1} \leq 250 \text{ MW}$$

$$20 \text{ MW} \leq P_{g2} \leq 100 \text{ MW}$$

$$30 \text{ MW} \leq P_{g3} \leq 90 \text{ MW}$$

- (a) If the lossless transmission lines are considered in this problem, determine the optimal dispatch of generation when the total system load is 170 MW. (10%)
- (b) For this problem, assume the real power loss is given by the simplified expression

$$P_L = 0.05P_{g1} + 0.04 P_{g2} + 0.07P_{g3} \quad (\text{MW})$$

Determine the optimal dispatch of generation when the total system load is 200 MW. (15%)

