

國立臺灣科技大學 110 學年度碩士班招生試題

系所組別：電機工程系碩士班丁二組
 科目：控制系統與數位邏輯

(總分為 100 分)

Problem 1: system transfer function with initial conditions (10 points)


Given a linear system with system input-output transfer function $T(s) = \frac{Y(s)}{U(s)} = \frac{1}{s(s^2 + 1)}$;
 compute output $y(t), t \geq 0$ with initial conditions: $y(0) = 1, \dot{y}(0) = -1, \ddot{y}(0) = 0$, and zero
 input, $u(t) = 0, t \geq 0$.

Problem 2: time and frequency responses (10 points)

Consider a control system with system transfer function $T(s) = \frac{Y(s)}{U(s)} = \frac{s + 2}{s^2 + 2s + 2}$; find
 frequency response bandwidth ω_{BW} and maximum overshoot $MO\%$ for unit-step response.

Problem 3: System block diagram (10 points)

Find the input-output transfer function $T(s) = Y(s)/R(s)$ of the system block diagram below.

 

Problem 4: Root-locus analysis (10 points)

Consider a negative unity-feedback system, $T(s) = \frac{L(s)}{1 + L(s)}$, with loop transfer function

$L(s) = \frac{8}{s(s + 2)(s + K)}$; draw the root-locus of $T(s)$ for $0 < K < \infty$. For higher score, the
 root-locus should be as detailed as possible.

Problem 5: Root-locus design (10 points)

Continue on Problem 4, design K such that the unit step response $y(t)$ of the closed-loop
 system, $T(s)$, having zero steady-state error $e_{ss} = \lim_{t \rightarrow \infty} (1 - y(t)) = 0$, zero maximum overshoot
 $MO = 0\%$ and 3dB bandwidth $\omega_{BW} \geq 0.5$ rad/sec.



國立臺灣科技大學 110 學年度碩士班招生試題

系所組別：電機工程系碩士班丁二組

科目：控制系統與數位邏輯

 
Problem 6 (10 points)Find $F(x, y, z)$ in Fig. 1. You must present the details.

Fig. 1. Logic circuit.


Problem 7 (12 points)

Draw the state diagram of the machine described by the following Verilog HDL.

```


module Problem_6(output reg y_out, input x_in, clk, reset);
  parameter s0=2'b00, s1=2'b01, s2=2'b10, s3=2'b11;
  reg [1:0] state, next_state;
  always@(posedge clk, negedge reset) //begin
  if (reset==1'b0) state <=s0; else state <= next_state;
  //end
  always@(state, x_in) begin
  y_out=0; next_state=0;
  case (state)
  s0: begin y_out=0; if (x_in) next_state=s1; else next_state=s0; end
  s1: begin y_out=0; if (x_in) next_state=s2; else next_state=s1; end
  s2: if (x_in) begin y_out=0; next_state=s3; end else begin y_out=1; next_state=s2; end
  s3: begin y_out=1; if (x_in) next_state=s0; else next_state=s1; end
  default: next_state=s0;
  endcase
  end
endmodule

```

 

 Problem 8 (13 points)

In Fig. 2, a 4-bit binary counter with Load (L), Count (C), data input $I_i, i = 0,1,2,3$, Clear, CLK, and output $A_i, i = 0,1,2,3$ is presented. Its function table is in Table 1. How to use and some logic gates to count from 0 to 134, and then back to 0.



Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

Fig. 2. 4-bit binary counter.

Table 1. Function table of 4-bit binary counter.

Problem 9 (15 points)

Consider the 4-bit (i.e., $A[3:0]$) up-down counter in Fig. 3. Given the following signals:

- (i) **initial begin** $CLK=1$; #5 forever $CLK=\sim CLK$; **end.**
- (ii) **initial fork** #10 $Reset_b=0$; #20 $Reset_b=1$; **join.**
- (iii) **initial fork** $Down=0$; $Up=0$; #40 $UP=1$; #150 $Down=1$; #200 $UP=0$; #250 $Down=0$; **join.**

Plot and explain the responses including, CLK , $Reset_b$, $Down$, Up , and $A[3:0]$ for a total of 300ns. (Plot: 10 pts ; Explain: 5 pts)

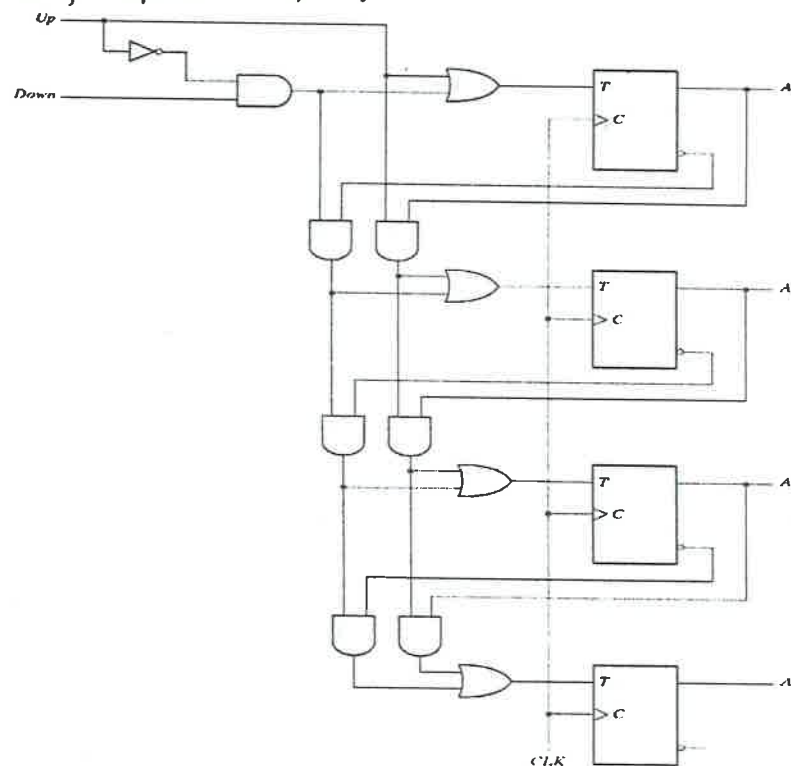


Fig. 3. 4-bit up-down counter.

