

# 國立臺灣科技大學

115學年度碩士班招生

## 試題

系所組別：0710電機工程系碩士班甲組

科 目：電力系統

<<507101>>



## 國立臺灣科技大學115學年度碩士班招生試題

系所組別：電機工程系碩士班甲組

科目：電力系統

(總分為100分;所有試題務必於答案卷內頁依序作答)

1. (30%) Figure 1 shows the oneline diagram of a three-phase power system. By selecting a common base of 100 MVA and 22 kV on the generator side, draw an impedance diagram showing all impedances including the load impedance in per-unit. (3% for each of  $G$ ,  $T_1$ ,  $T_2$ ,  $T_3$ ,  $T_4$ ,  $M$ ; 4% for each of *Line 1*, *Line 2*, *Load*). The data are given as follows:

$G$ :	90 MVA	22 kV	$x = 0.18$ per unit
$T_1$ :	50 MVA	22/220 kV	$x = 0.10$ per unit
$T_2$ :	40 MVA	220/11 kV	$x = 0.06$ per unit
$T_3$ :	40 MVA	22/110 kV	$x = 0.064$ per unit
$T_4$ :	40 MVA	110/11 kV	$x = 0.08$ per unit
$M$ :	66.5 MVA	10.45 kV	$x = 0.185$ per unit

Lines 1 and 2 have series reactances of 48.4 and 65.43  $\Omega$ , respectively. At bus 4, the three-phase load absorbs 57 MVA at 10.45 kV and 0.6 power factor lagging.

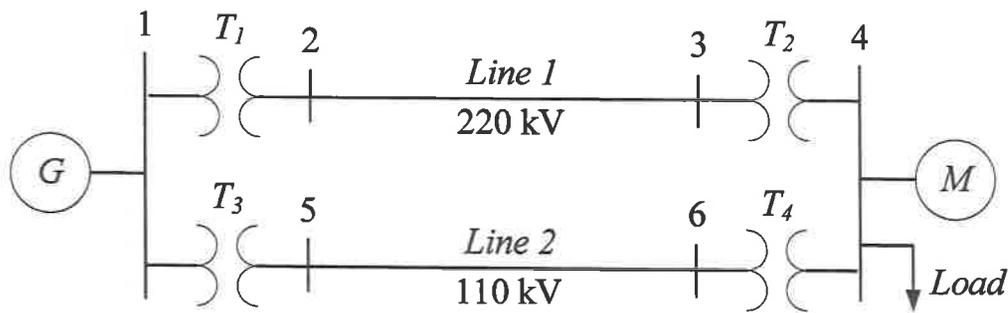


Figure 1

2. (20 %) A 69-kV, three-phase short transmission line is 16 km long. The line has a per phase series impedance of  $0.125 + j0.4375 \Omega$  per km. Determine the sending end voltage, voltage regulation, the sending end power, and the transmission efficiency when the line delivers
- (a) (10%) 70 MVA, 0.8 lagging power factor at 64 kV.
- (b) (10%) 120 MW, unity power factor at 64 kV.



## 國立臺灣科技大學115學年度碩士班招生試題

系所組別： 電機工程系碩士班甲組

科 目： 電力系統

(總分為100分;所有試題務必於答案卷內頁依序作答)

3. (20%) A three-phase, 60-Hz synchronous machine is driven at constant synchronous speed by a prime mover. The armature windings are initially open-circuited and field voltage is adjusted so that the armature terminal voltage is at the rated value (i.e., 1.0 per unit). The generator is suddenly subjected to a symmetrical three-phase short circuit at the instant when direct axis is along the magnetic axis of phase  $a$ , i.e.,  $\delta = 0$ . An oscillogram of the short-circuited current is obtained. The peak values at the first two cycles, at the 20<sup>th</sup> and 21<sup>st</sup> cycles, and the steady value after a long time were recorded as tabulated in the following table.

	1 <sup>st</sup> cycle	2 <sup>nd</sup> cycle	...	20 <sup>th</sup> cycle	21 <sup>st</sup> cycle	...	Steady state
$I_{max}$ , pu	8.7569	6.7363	...	2.8893	2.8608	...	1.1785
Time, sec	0.0042	0.0208	...	0.3208	0.3375	...	5.0000

Determine the transient reactance and time constant (20%).

4. (30%) A 60-Hz synchronous generator having inertia constant  $H = 5$  MJ/MVA and a direct axis transient reactance  $X'_d = 0.3$  per unit is connected to an infinite bus through a purely reactive circuit as shown in Figure 2. Reactances are marked on the diagram on a common system base. The generator is delivering real power  $P_e = 0.8$  per unit and  $Q = 0.074$  per unit to the infinite bus at a voltage of  $V = 1$  per unit.

(a) A temporary three-phase fault occurs at the sending end of the line at point  $F$ . When the fault is cleared, both lines are intact. Determine the critical clearing angle and the critical fault clearing time (20%).

(b) A three-phase fault occurs at the middle of one of the lines, the fault is cleared, and the faulted line is isolated. Determine the critical clearing angle (10%).

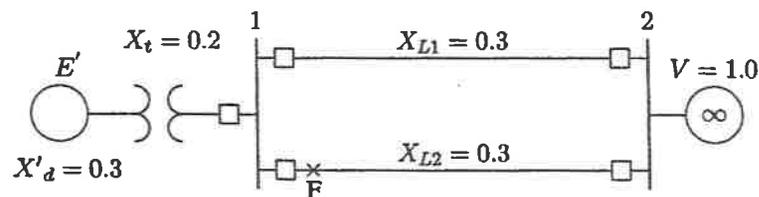


Figure 2 One-line diagram for Problem 4.

