

國立臺灣科技大學
八十七學年度碩士班招生考試試題

所 別： 電子工程技術研究所
學程別：

組 別： 元件與材料組

科 目： 電子電路學

1. Assume the B-E cut-in voltage for the transistor is 0.7 V, the C-E saturation voltage is 0.2 V for every transistor.

(a) The measured value of V_C is 6.34 V. Determine I_B , I_E , I_C , V_{CE} and β for the circuit shown in Figure 1. (10%)

(b) Consider the circuit shown in Figure 2. Let $\beta = 150$, $R_E = 0.2$ K Ω , and $R_C = 1$ K Ω . Find R_1 , R_2 such that the bias is stable and the quiescent output voltage is 0V. (10%)

Hint: for good bias stability $R_B \ll (1+\beta)R_E$.

Set $R_B = 0.1(1+\beta)R_E$ $R_B = R_1 \parallel R_2$

(c) Assuming $\beta = 50$, determine I_{BQ} , I_{CQ} , and V_{CEQ} for the circuit shown in Figure 3. (10%)

(d) Assume C is short to a-c signal. Determine the voltage gain, and input impedance for the circuit shown in Figure 3. (10%)

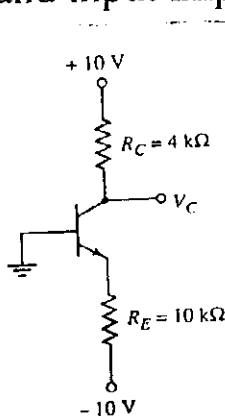


Figure 1

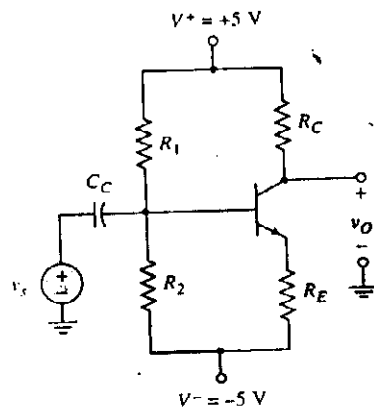


Figure 2

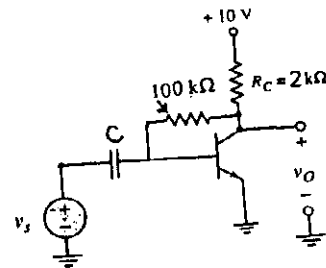


Figure 3

2. For the NMOS common-source amplifier shown in Figure 4, the transistor parameters are: $V_{Th} = 2V$, $K_n = 1$ mA/V², and $\lambda = 0$. The circuit parameters are $V_{DD} = 12V$, $R_S = 2K\Omega$, $R_D = R_L = 3K\Omega$, $R_1 = 300K\Omega$, and $R_2 = 200K\Omega$.

(a) Determine the quiescent values of I_D and V_{DS} . (5%)

(b) Find the small-signal voltage gain. (5%)

(c) Determine the maximum symmetrical swing in the output voltage. (10%),

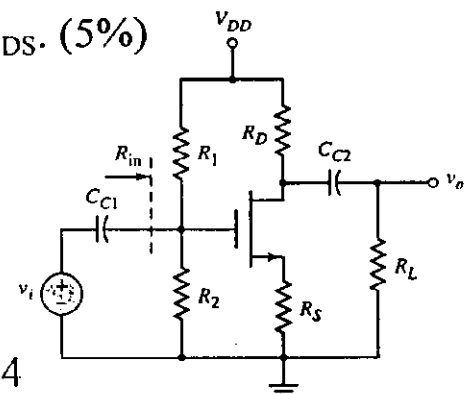


Figure 4

國立臺灣科技大學
八十七學年度碩士班招生考試試題

所 別： 電子工程技術研究所
學程別：

組別： 元件與材料組

科目： 電子電路學

3. For the circuit shown in Figure 5, the transistor parameters are:
 $V_{ThD} = 1V$, $V_{ThL} = -1V$, $K_{nD} = 1 \text{ mA/V}^2$, $K_{nL} = 0.2 \text{ mA/V}^2$, and
 $\lambda_D = \lambda_L = 0.01 \text{ V}^{-1}$. Assume the circuit is biased at $V_{DD} = 5V$.

(a) Analyze whether M_D and M_L are in saturation region or nonsaturation region when V_{GSD} increase from 0V to V_{DD} . Draw the voltage transfer characteristic curve. (10%)

(b) Find V_{GSD} and I_{DQ} such that the Q-point is in the middle of the saturation region. (10%)

(c) Determine the small-signal voltage gain. (5%)

Remark: M_L is a N-channel depletion mode MOSFET

M_D is a N-channel enhancement mode MOSFET

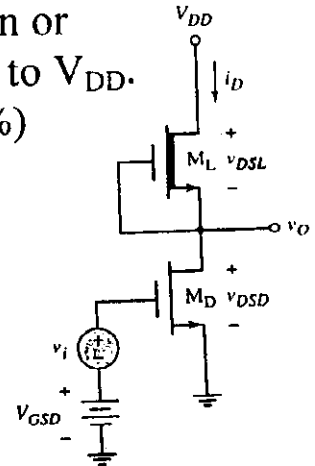


Figure 5

4. For the circuit shown in Figure 6, the parameters are: $R_S = 0.1 \text{ K}\Omega$, $R_1 = 20 \text{ K}\Omega$, $R_2 = 2.2 \text{ K}\Omega$, $R_E = 0.1 \text{ K}\Omega$, $R_C = 2 \text{ K}\Omega$, $C_C = 47 \mu\text{F}$, and $V_{CC} = 10V$. The transistor parameters are $V_{BE(ON)} = 0.7 \text{ V}$, $\beta = 200$, and $V_A = \infty$.

(a) Determine the corner frequency. (5%)

(b) Calculate the midband gain. (5%)

(c) Draw Bode plots for this circuit. (5%)

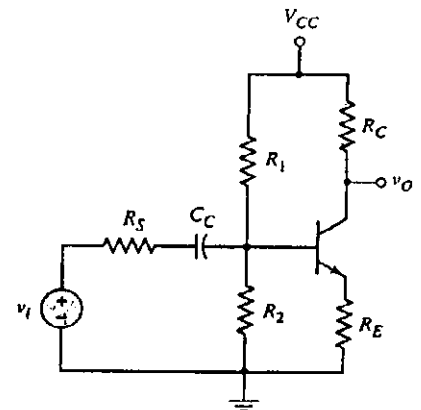


Figure 6