

國立臺灣科技大學
八十八學年度碩士班招生考試試題

系所別：電機工程系碩士班

組別：乙組

科目：電子學

1. Consider the modified difference amplifier in Figure 1. Find the differential voltage gain v_o/v_d . (10%)

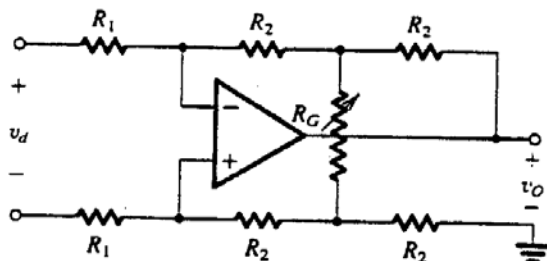


Figure 1.

2. For the follower circuit in Figure 2, let transistor Q_1 have $\beta = 20$ and transistor Q_2 have $\beta = 200$, and neglect the effect of r_o . Use $V_{BE} = 0.7$ volts.
- (1) Find the dc emitter current of Q_1 and Q_2 . Also find the dc voltage V_{B1} and V_{B2} . (4%)
 - (2) If a load resistance $R_L = 1\text{ k}\Omega$ is connected to the output terminal, find the voltage gain from the base to the emitter of Q_2 , v_o/v_{b2} , and find the input resistance R_{ib2} looking into the base of Q_2 . (4%)
 - (3) Replacing Q_2 with its input resistance R_{ib2} found in (2), analyze the circuit of emitter follower Q_1 to determine its input resistance R_i , and the gain from its base to its emitter, v_{e1}/v_{b1} . (4%)
 - (4) If the circuit is fed with a source having a $100\text{ k}\Omega$ resistance, find the transmission to the base of Q_1 , v_{b1}/v_s . (4%)
 - (5) Find the overall voltage gain v_o/v_s . (4%)

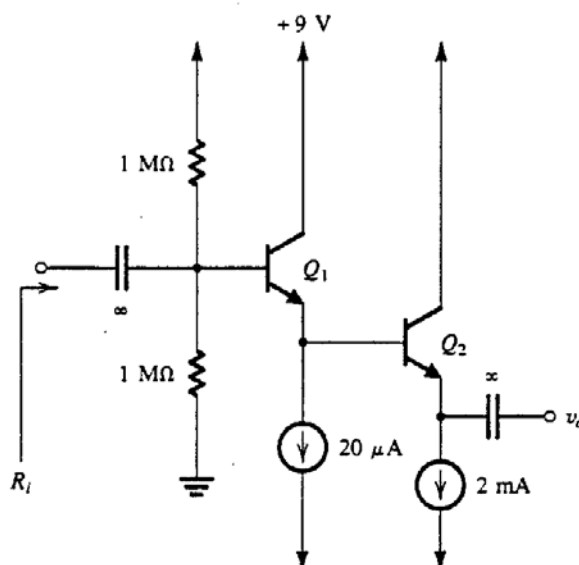


Figure 2.

國立臺灣科技大學
八十八學年度碩士班招生考試試題

系所別：電機工程系碩士班

組別：乙組

科目：電子學

3. The differential amplifier circuit in Figure 3 utilizes a resistor connected to the negative power supply to establish the bias current I .

- (1) For $v_{B1} = v_d/2$ and $v_{B2} = -v_d/2$ where v_d is a small signal with zero average. Find the magnitude of the differential gain, $|v_o/v_d|$. (5%)
- (2) For $v_{B1} = v_{B2} = v_{CM}$, find the magnitude of the common-mode gain, $|v_o/v_{CM}|$. (5%)
- (3) Calculate the CMRR. (5%)
- (4) If $v_{B1} = 0.1\sin 2\pi \times 60t + 0.005\sin 2\pi \times 1000t$, volts, $v_{B2} = 0.1\sin 2\pi \times 60t - 0.005\sin 2\pi \times 1000t$, volts, find v_o . (5%)

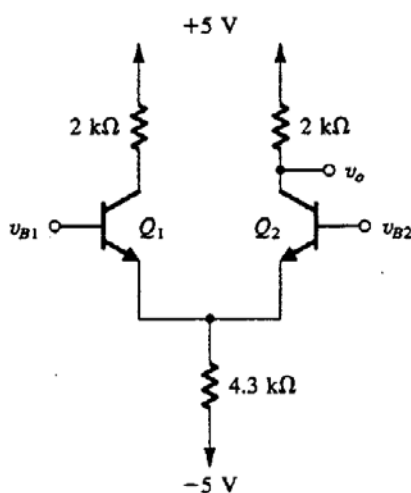


Figure 3

國立臺灣科技大學
八十八學年度碩士班招生考試試題

系所別：電機工程系碩士班

組別：乙組

科目：電子學

4. A differential amplifier having a transfer function $A(s) = \frac{1000}{(1 + \frac{s}{2\pi \times 10^6})(1 + \frac{s}{2\pi \times 10^7})}$ is connected as a

differentiator which is shown in Figure 4.

(a) On the basis of the rate-of-closure rule, what is the smallest time-constant RC for which operation is stable? (15%)

(b) What is the corresponding approximate phase margin?(5%)

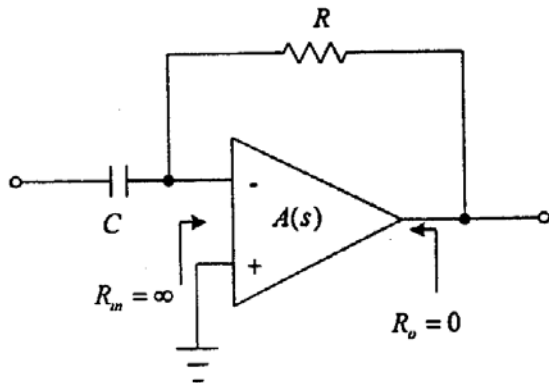


Figure 4

5. For the circuit in Figure 5, let Q_1 and Q_2 be identical, $\beta = 100$, $C_\mu = 2pF$, and $f_T = 400MHz$. The small signal equivalent circuit of Figure 5 is shown in Figure 6.

(a) Calculate the values of r_π , g_m , and C_x .(10%)

(b) Calculate the midband voltage gain and the upper 3-dB frequency.(10%)

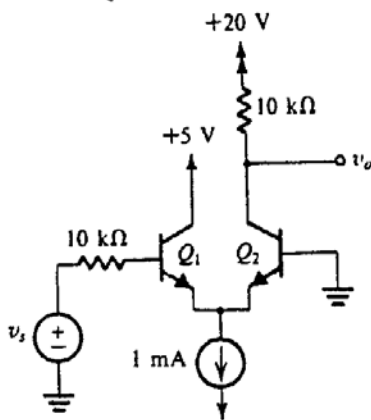


Figure 5

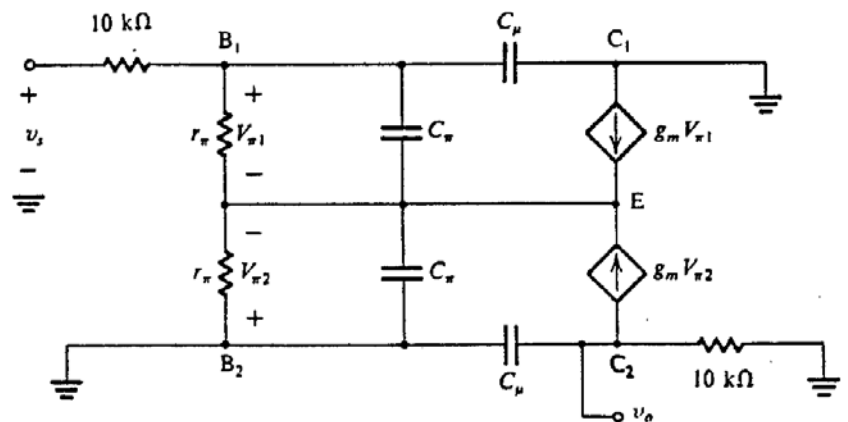


Figure 6.

6. Explain (a) all-pole filter and (b) input bias current of an op amp.(10%)