

國立臺灣科技大學

八十九學年度碩士班招生考試試題

系所組別：電子工程系乙一組、電子工程系乙二組、電子工程系乙三組

科目：電子電路學

(總分共 100 分)

注意：1-4 題均屬於填充題，每空格為五分，請在分析後，保留推導結果，依子題順序將答案填寫在答案卷上；單位必需填寫否則不予計分。

1. A bridged-T network is placed in the negative-feedback path of an infinite-gain op amp as shown in Fig. P1. Please analyze this circuit and then write down the results of the following problems in order on the answer sheet. (25%)

(注意：請分析後，保留推導結果並依序寫下答案，且必需有單位，否則不予計分)

(1) Find the transfer function

$$T(s) = V_o(s)/V_i(s) = \underline{\hspace{2cm}}$$

(2) What kind of the filter in this amplifier?

That is

(3) Find its ω_o ,

$$\omega_o = \underline{\hspace{2cm}}$$

(4) Find its Q ,

$$Q = \underline{\hspace{2cm}}$$

(5) Find the center-frequency gain of this amplifier

$$|T(j\omega_o)| = \underline{\hspace{2cm}}$$

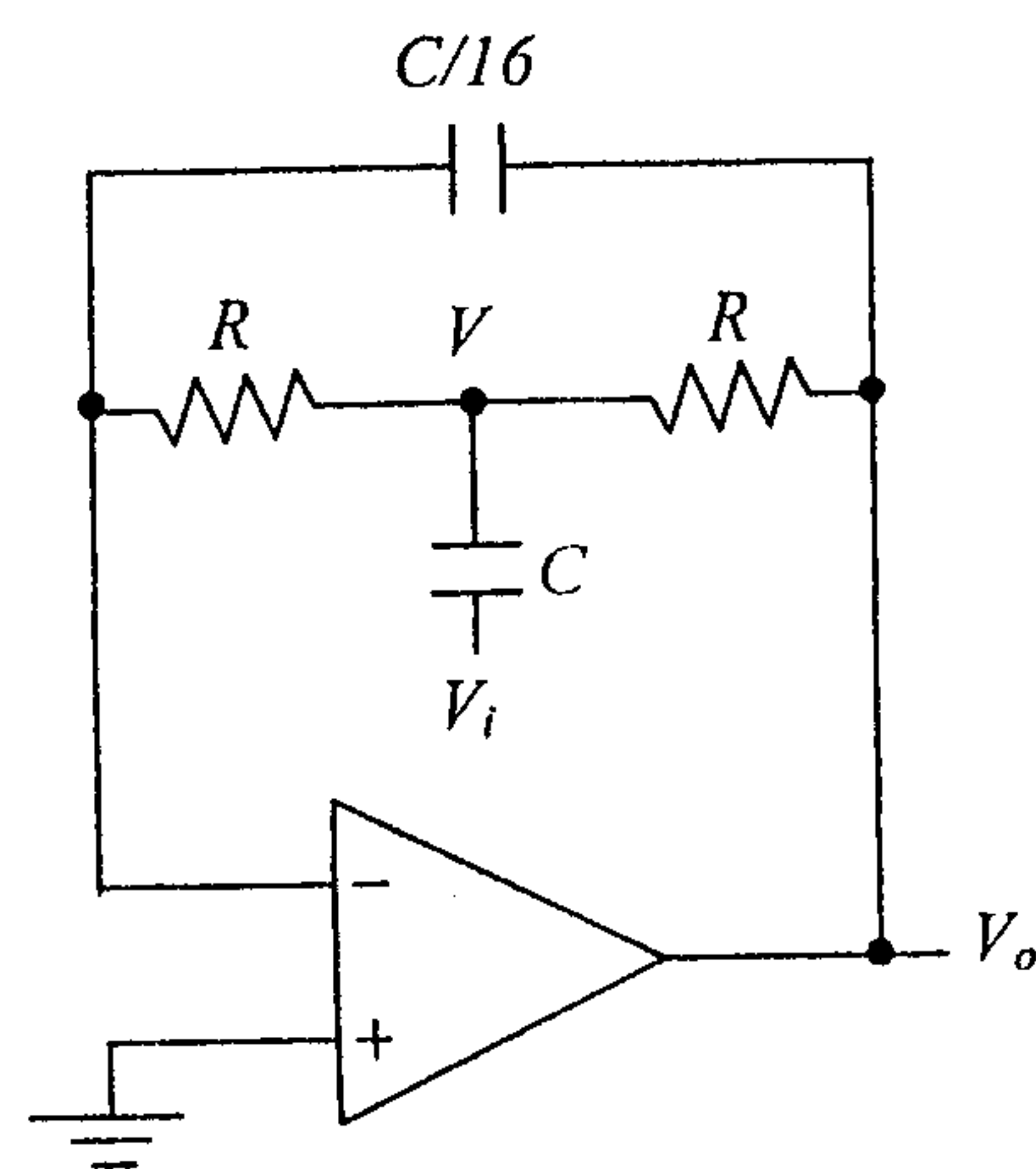


Fig. P1

2. An FET amplifier is shown in Fig. P2 is biased to operate at $I_D = 1\text{mA}$ and $g_m = 1\text{mA/V}$. Neglecting r_o , answer the following problems. Please analyze this circuit and then write down the results of the following problems in order on the answer sheet. (25%)

(注意：請分析後，保留推導結果並依序寫下答案，且必需有單位，否則不予計分)

(6) Find the midband gain

$$A_M = \underline{\hspace{2cm}}$$

(7) Find the value of C_S that places the corresponding pole at 10Hz



國立臺灣科技大學

八十九學年度碩士班招生考試試題

系所組別：電子工程系乙一組、電子工程系乙二組、電子工程系乙三組

科目：電子電路學

$$C_S = \underline{\hspace{2cm}}$$

- (8) What is the frequency of the transfer-function zero introduced by C_S ?

$$f_z = \underline{\hspace{2cm}}$$

- (9) Find the transfer function

$$V_o(s)/V_i(s) = \underline{\hspace{2cm}}$$

- (10) Find the dc gain of this amplifier

$$G_{dc} = V_o(0)/V_i(0) = \underline{\hspace{2cm}}$$

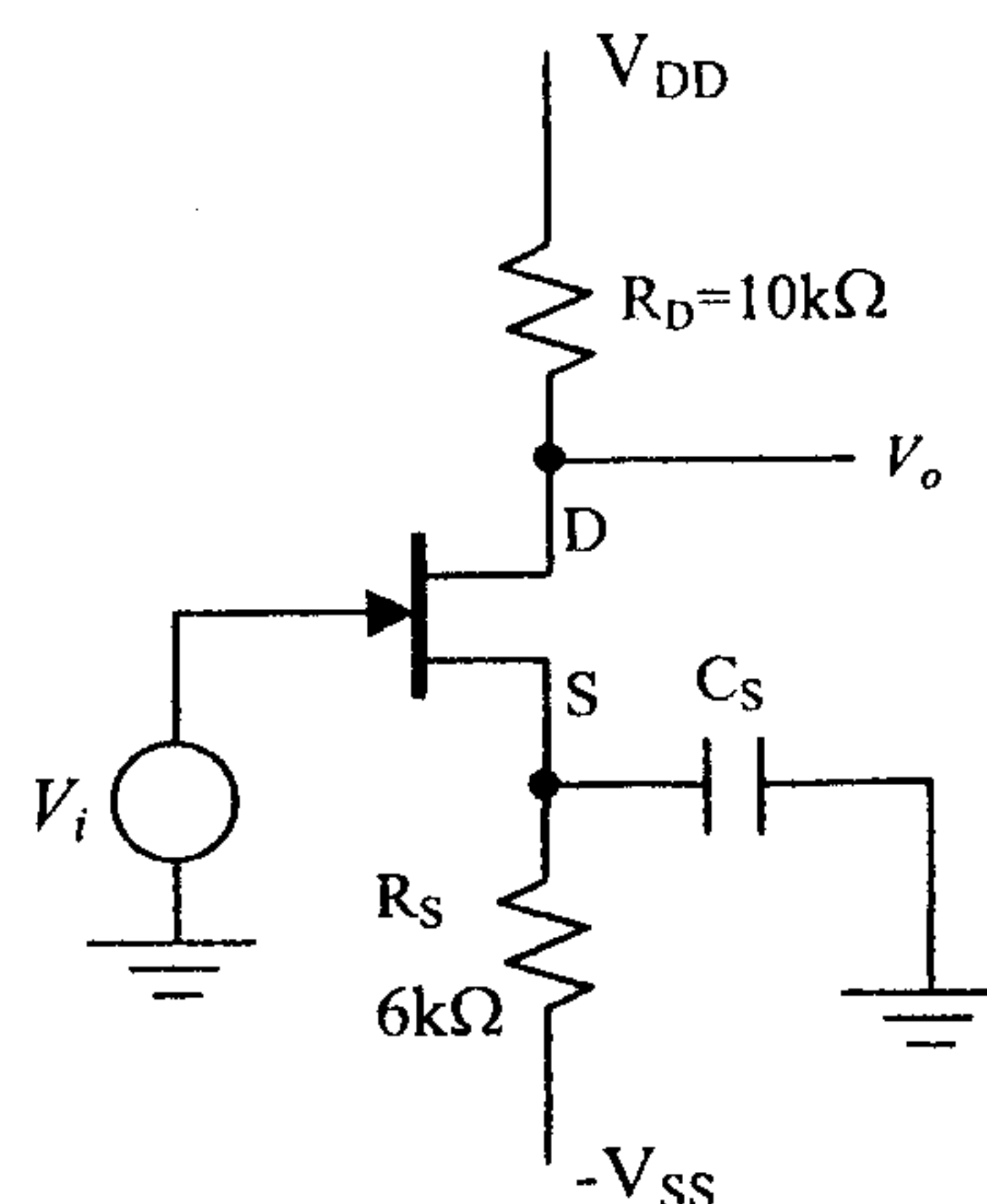


Fig. P2

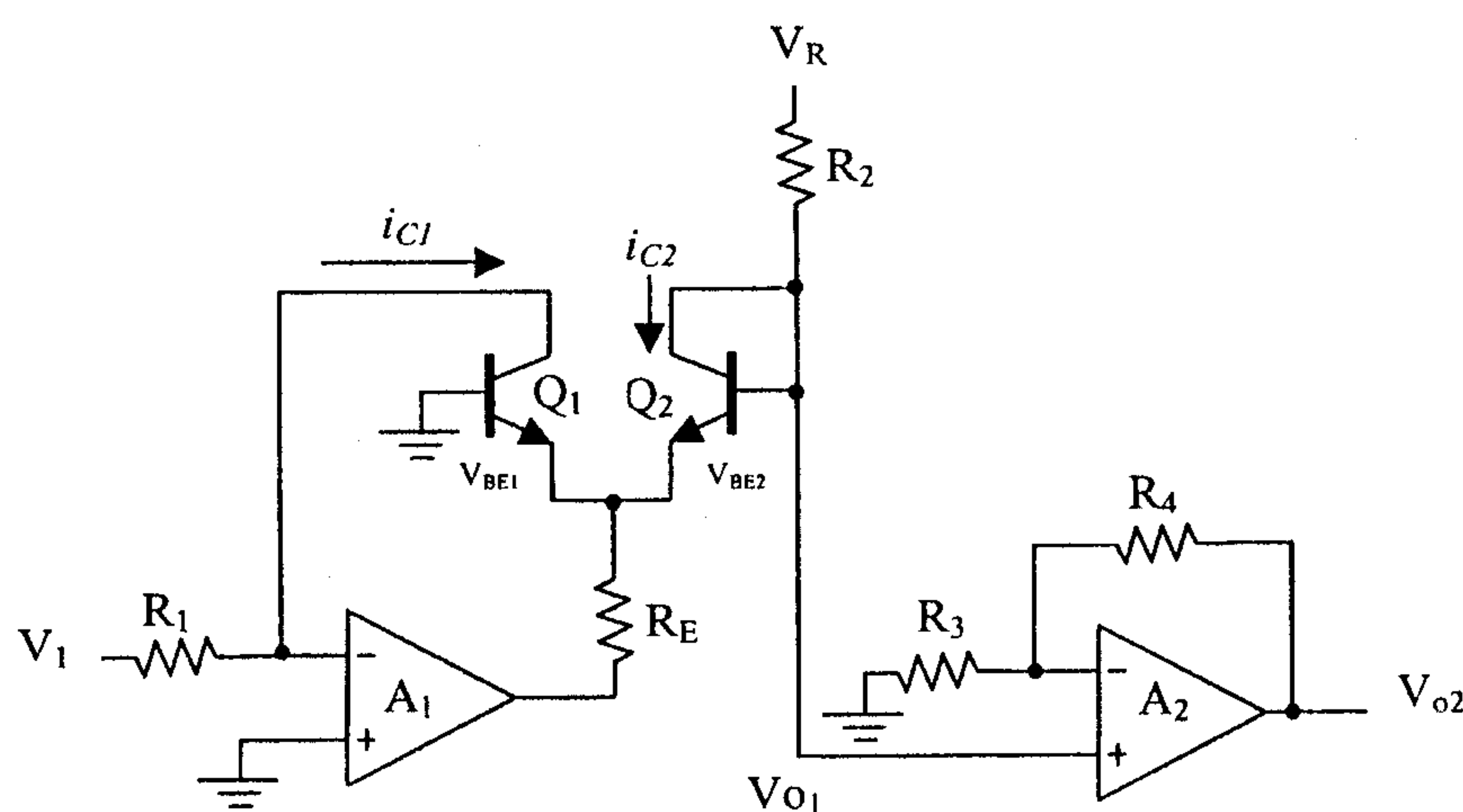


Fig. P3



3. A Log amplifier to be implemented by two op-amps and two transistors is shown in Fig. P3, in which all devices are identical. Some parameters including a reference voltage V_R , thermal voltage V_T , and reverse saturation current I_S are considered. If the input voltage is V_i , please analyze this circuit and then write down the results of the following problems in order on the answer sheet. (25%)

(注意：請分析後，保留推導結果並依序寫下答案，且必需有單位，否則不予計分)

- (11) Find the current i_{C2} in terms of the specified parameters

國立臺灣科技大學

八十九學年度碩士班招生考試試題

系所組別：電子工程系乙一組、電子工程系乙二組、電子工程系乙三組

科目：電子電路學

$$i_{C2} = \underline{\hspace{2cm}}$$

- (12) Find the voltage V_o in terms of the specified parameters

$$V_{o1} = \underline{\hspace{2cm}}$$

- (13) Find the voltage V_{o2} in terms of the specified parameters

$$V_{o2} = \underline{\hspace{2cm}}$$

- (14) Let $R_1=R_2=R_3=10\text{k}\Omega$, $R_4=375\text{k}\Omega$, and $V_R=10\text{V}$. If $T=300\text{K}$, determine the output voltage V_{o2} for $V_I=0.02\text{V}$ and 2.0V .

$$V_{o2} = \underline{\hspace{2cm}} \text{ for } V_I=0.02\text{V},$$

$$V_{o2} = \underline{\hspace{2cm}} \text{ for } V_I=2.0\text{V}.$$

4. A Class A power amplifier is shown in Fig. P4a, in which the transistor have the specifications, i.e., $P_{C,max}=10\text{W}$ (after derating), $BV_{CEO}=60\text{V}$, and $i_{C,max}=3\text{A}$. In this problem, $R_E=1\Omega$, $R_L=8\Omega$, the reactance's of all capacitors are neglected, and the inductance is ∞ . If the input signal is sinusoidal, please analyze this circuit and then write down the results of the following problems in order on the answer sheet.(25%)

(注意：請分析後，保留推導結果並依序寫下答案，且必需有單位，否則不予計分)

- (15) Find the optimal operating point of the transistor to achieve a maximum symmetrical swing

$$(I_{CQ}, V_{CEQ}) = (\underline{\hspace{2cm}})$$

- (16) Plot the $P_{C,max}$ curve on the output characteristic curve of i_C-v_{CE} shown in Fig. P4b and find the possible supply voltage V_{CC} in this circuit,

繪製 $P_{C,max}$ curve 在如 Fig. 4b 之 i_C-v_{CE} 座標上 (此作圖為五分)

$$V_{CC} = \underline{\hspace{2cm}}$$

- (17) Find the maximum output power $P_{L,ac,max}$ for a sinusoidal input signal

$$P_{L,ac,max} = \underline{\hspace{2cm}}$$

- (18) Find the maximum power $P_{CC,max}$ drawn from the power supply and the maximum power efficiency η_{max} in this amplifier

$$P_{CC,max} = \underline{\hspace{2cm}}$$



國立臺灣科技大學
八十九學年度碩士班招生考試試題
系所組別： 電子工程系乙一組、電子工程系乙二組、電子工程系乙三組
科 目： 電子電路學

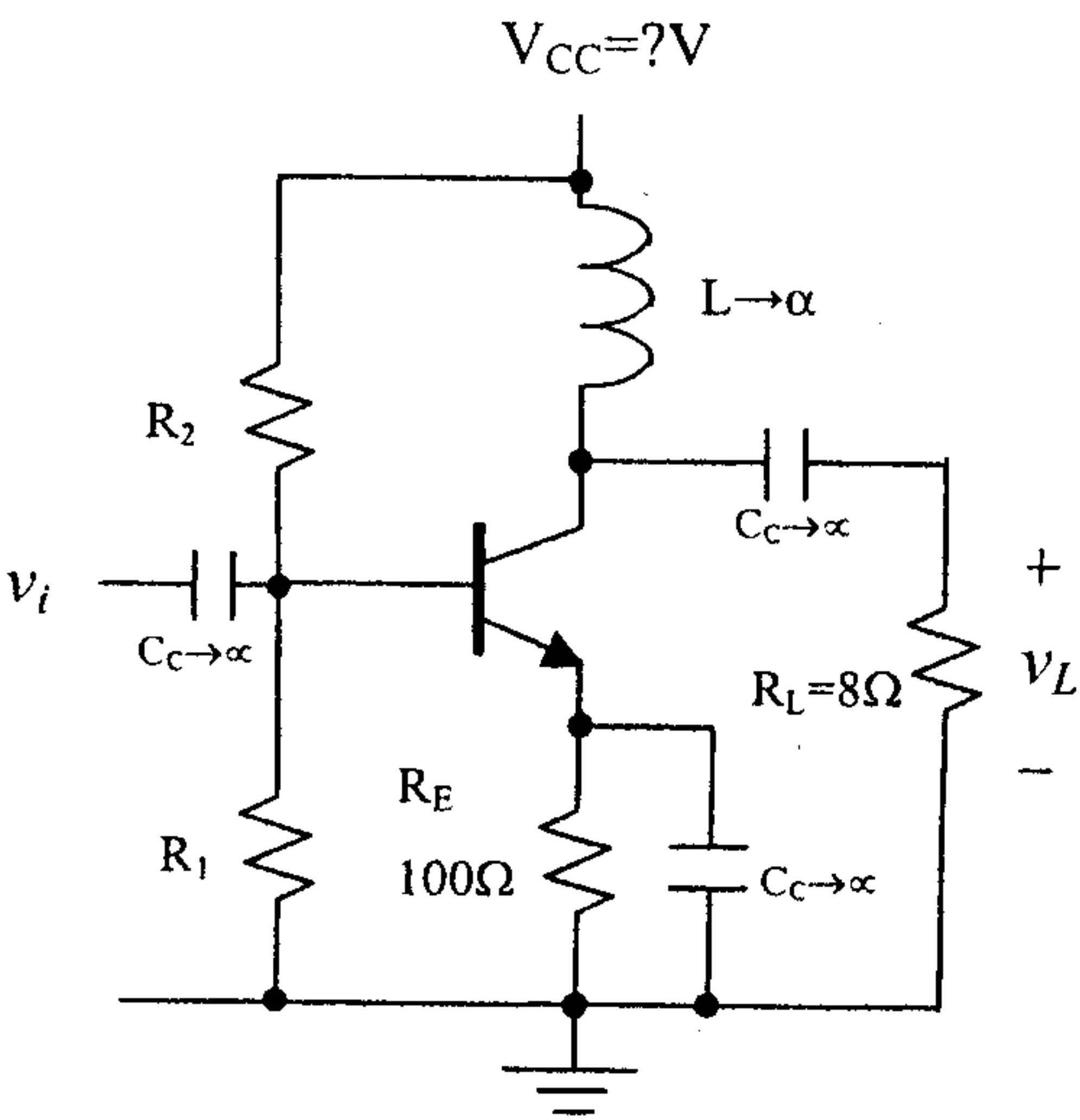


Fig. P4a

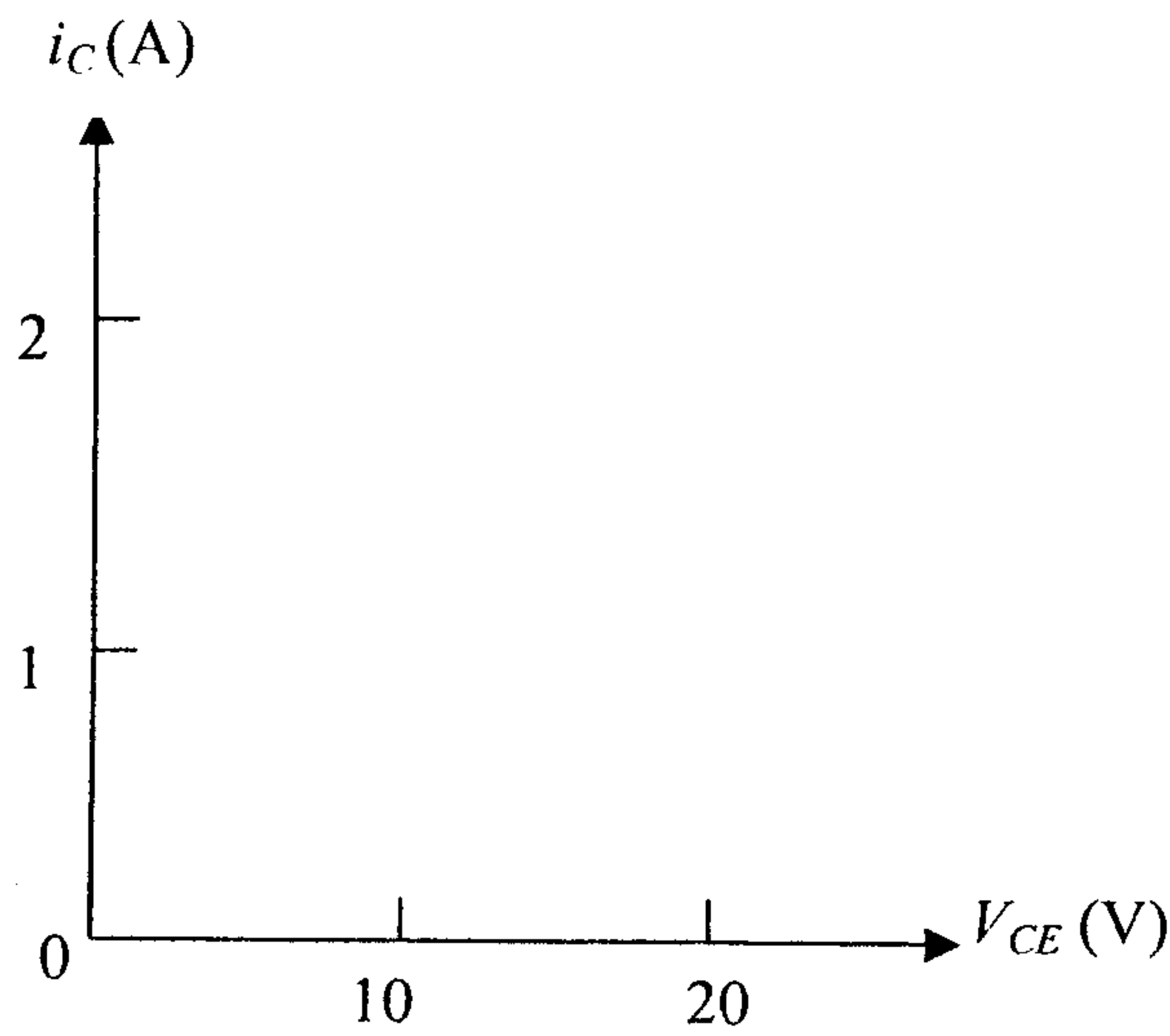


Fig. P4b

