

國立臺灣科技大學
八十九學年度碩士班招生考試試題

系所組別：電機工程系甲組

科 目：電路學

1. The transmission matrix T is defined by
$$\begin{bmatrix} \bar{V}_1 \\ \bar{I}_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} \bar{V}_2 \\ \bar{I}_2 \end{bmatrix} = T \begin{bmatrix} \bar{V}_2 \\ \bar{I}_2 \end{bmatrix}.$$

(a) Find T for the two-port network shown in Fig. 1 under sinusoidal steady-state conditions and the angular frequency $\omega = 1000 \text{ rad./s.}$ (15%)

(b) Find the open-circuit voltage transfer function $H \triangleq \left. \frac{\bar{V}_2}{\bar{V}_1} \right|_{\bar{I}_2 = 0}$. (5%)

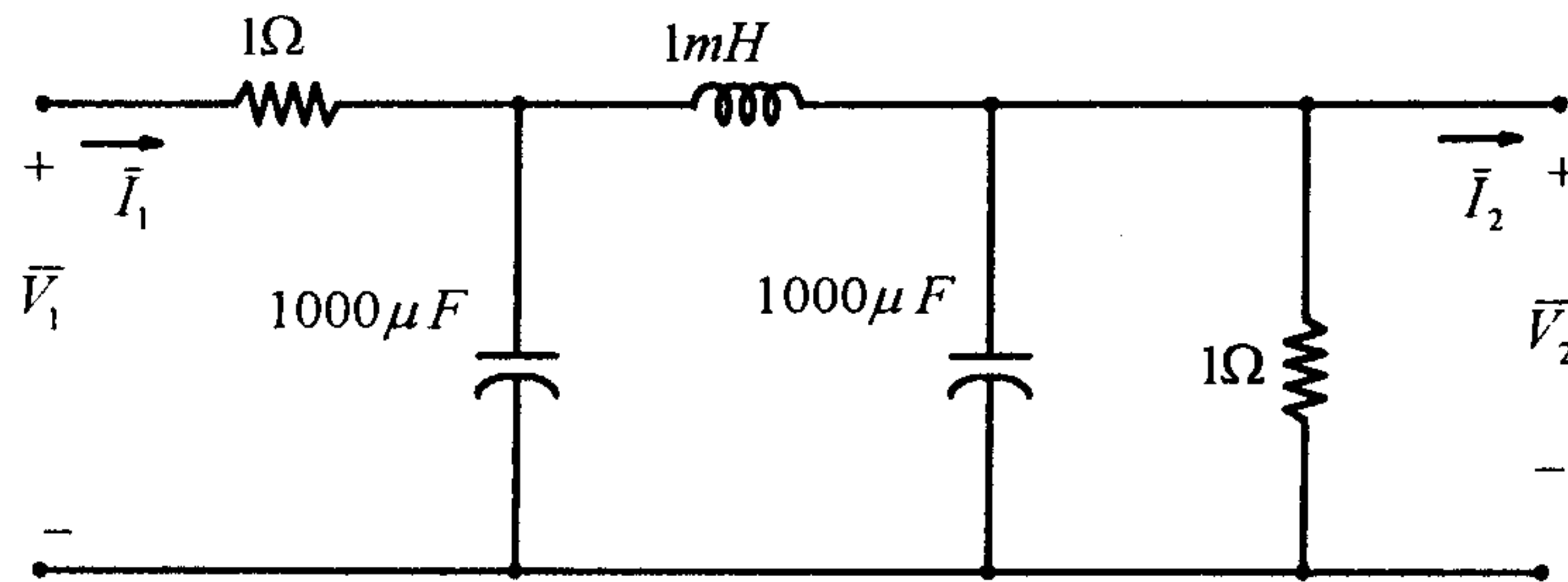


Fig. 1

2. Consider the circuit shown in Fig. 2.

(a) Write the state equation in matrix form
$$\begin{bmatrix} \frac{di_L}{dt} \\ \frac{dv_c}{dt} \end{bmatrix} = A \begin{bmatrix} i_L \\ v_c \end{bmatrix} + B v_s.$$
 (10%)

(b) Find the transfer function $\frac{V_c(s)}{V_s(s)}$. Let $V_c(s)$ and $V_s(s)$ be the Laplace transform of v_c and v_s , respectively. (10%)

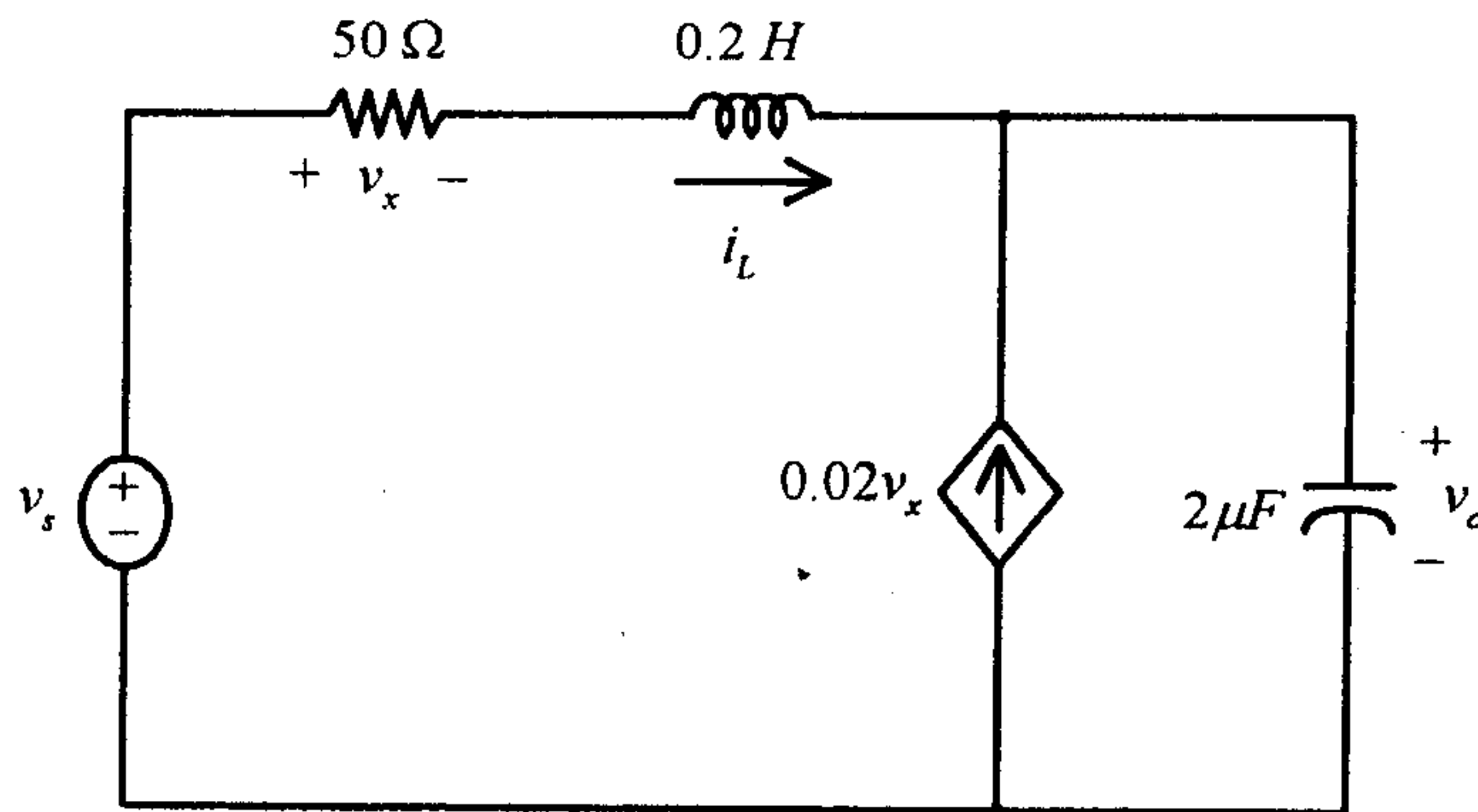


Fig. 2



國立臺灣科技大學
八十九學年度碩士班招生考試試題

系所組別：電機工程系甲組
科目：電路學

3. For the ideal op-amp circuit shown in Fig. 3, the initial conditions are $v_a(0^+) = 0V$ and $v_b(0^+) = 5V$. Determine the output voltage $v_o(t)$ for $t > 0$ with $R = 100K\Omega$ and $C = 1\mu F$. (20%)

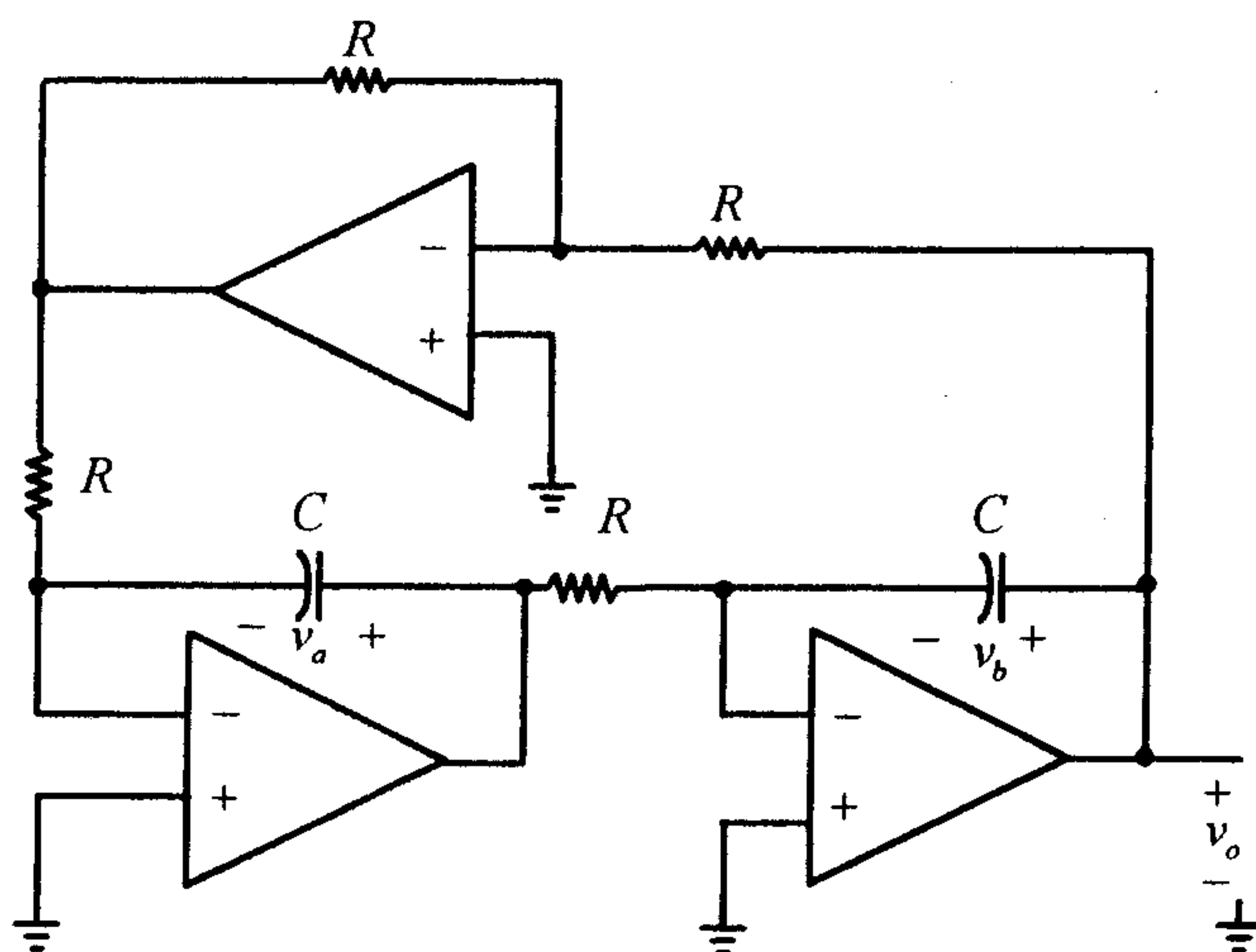


Fig. 3

4. In the circuit of Fig. 4, $R_1 = 2\Omega$, $R_2 = 0.12\Omega$, $j\omega L_1 = j8\Omega$, $j\omega L_2 = j0.45\Omega$, $j\omega M = j1.7\Omega$, $\bar{Z}_s = 1 + j1\Omega$, $\bar{Z}_L = 2 - j1\Omega$ and $|\bar{V}_s| = 400V$ (rms).

- (a) Find the current $|\bar{I}_1|$ and $|\bar{I}_2|$. (12%)
(b) Calculate the average power delivered to the load \bar{Z}_L . (8%)

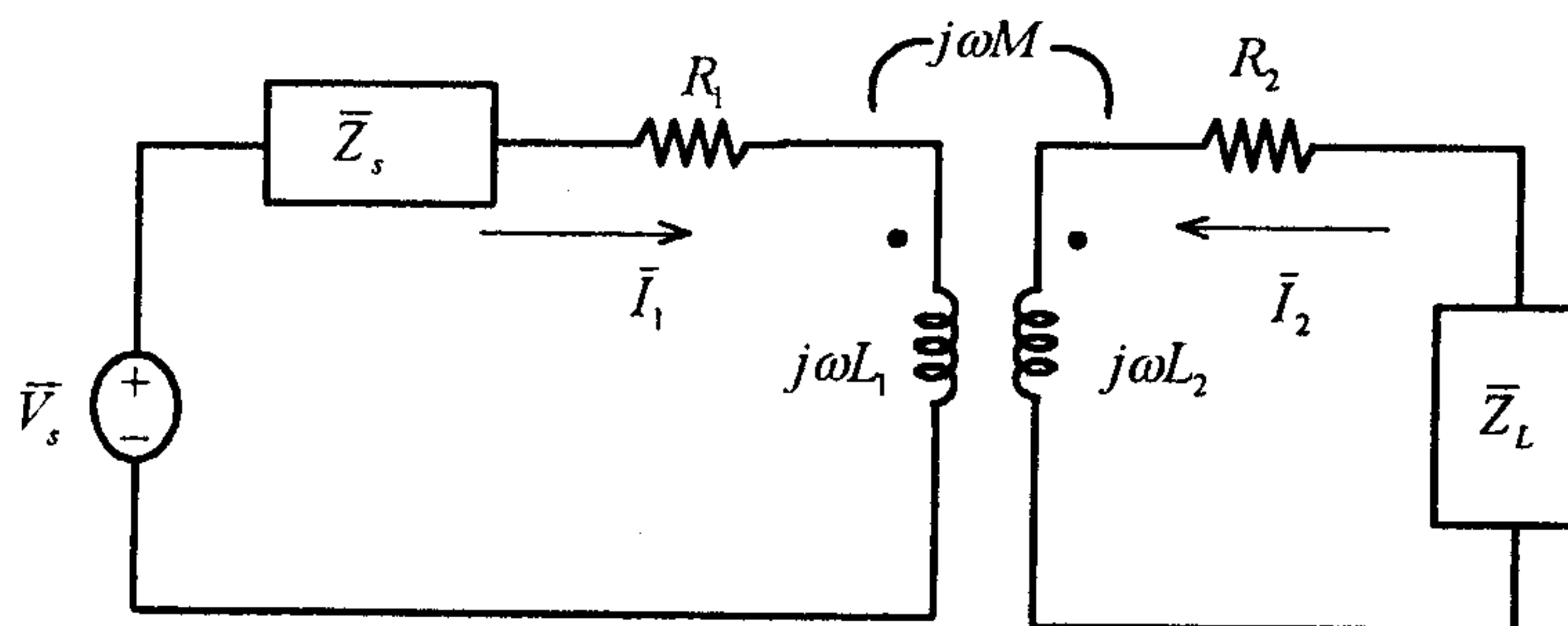


Fig. 4



國立臺灣科技大學
八十九學年度碩士班招生考試試題

系所組別：電機工程系甲組

科目：電路學

5. Two wattmeters are connected to the balanced three-phase load as shown in Fig. 5. The line voltage in the balanced positive (abc)-sequence source is $\bar{V}_{ab} = 480\angle 0^\circ V$ (rms).

- Determine the two wattmeter readings (W_1, W_2). (10%)
- Calculate the real power absorbed by the total load. (5%)
- Calculate the power factor of the total load. (5%)

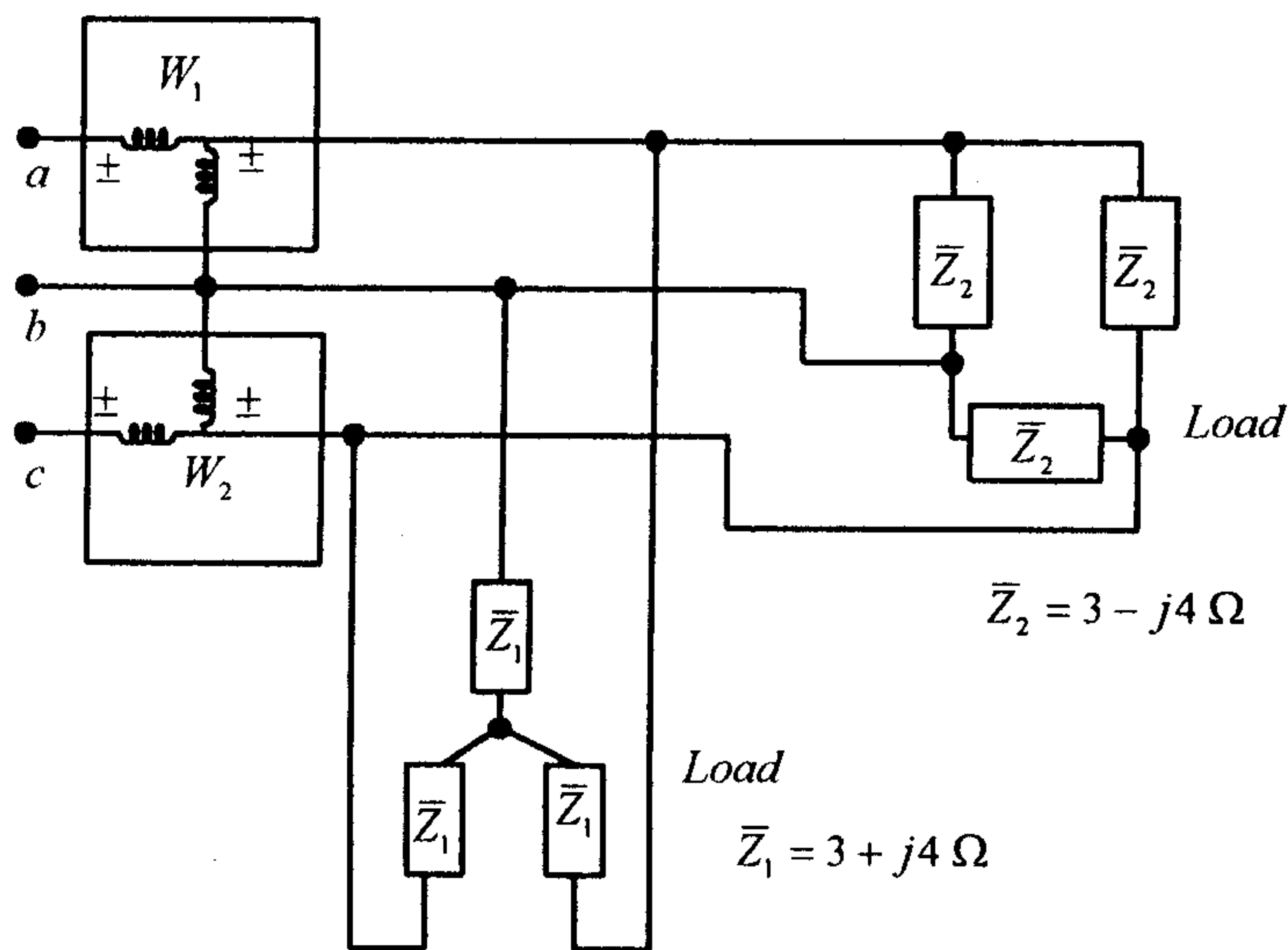


Fig.5

