

國立臺灣科技大學
九十學年度碩士班招生考試試題

系所組別：電機工程系甲組
科目：電路學

電路學總分 100 分，共五題，每題 20 分。

- For the circuit shown in Fig.P.1, set up the mesh-current equation for the circuit, then solve the current flowing in every branch. Draw the circuit and write all the branch currents in polar form on the circuit. (20 %)


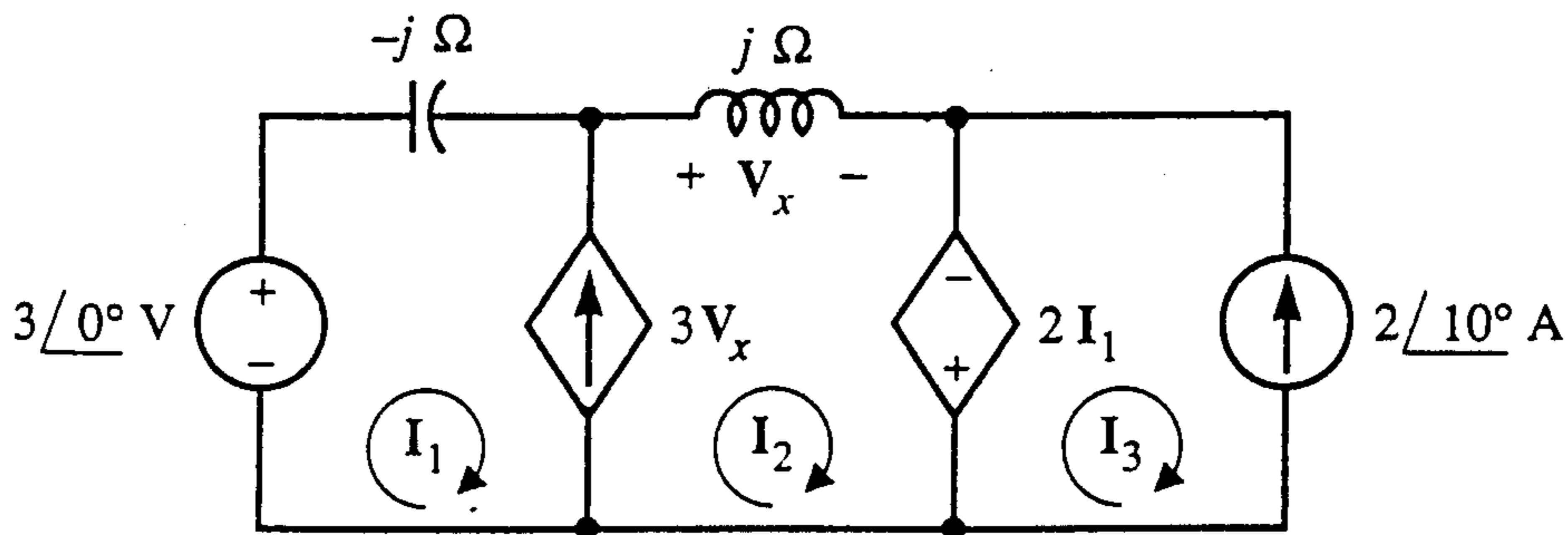


Fig.P.1

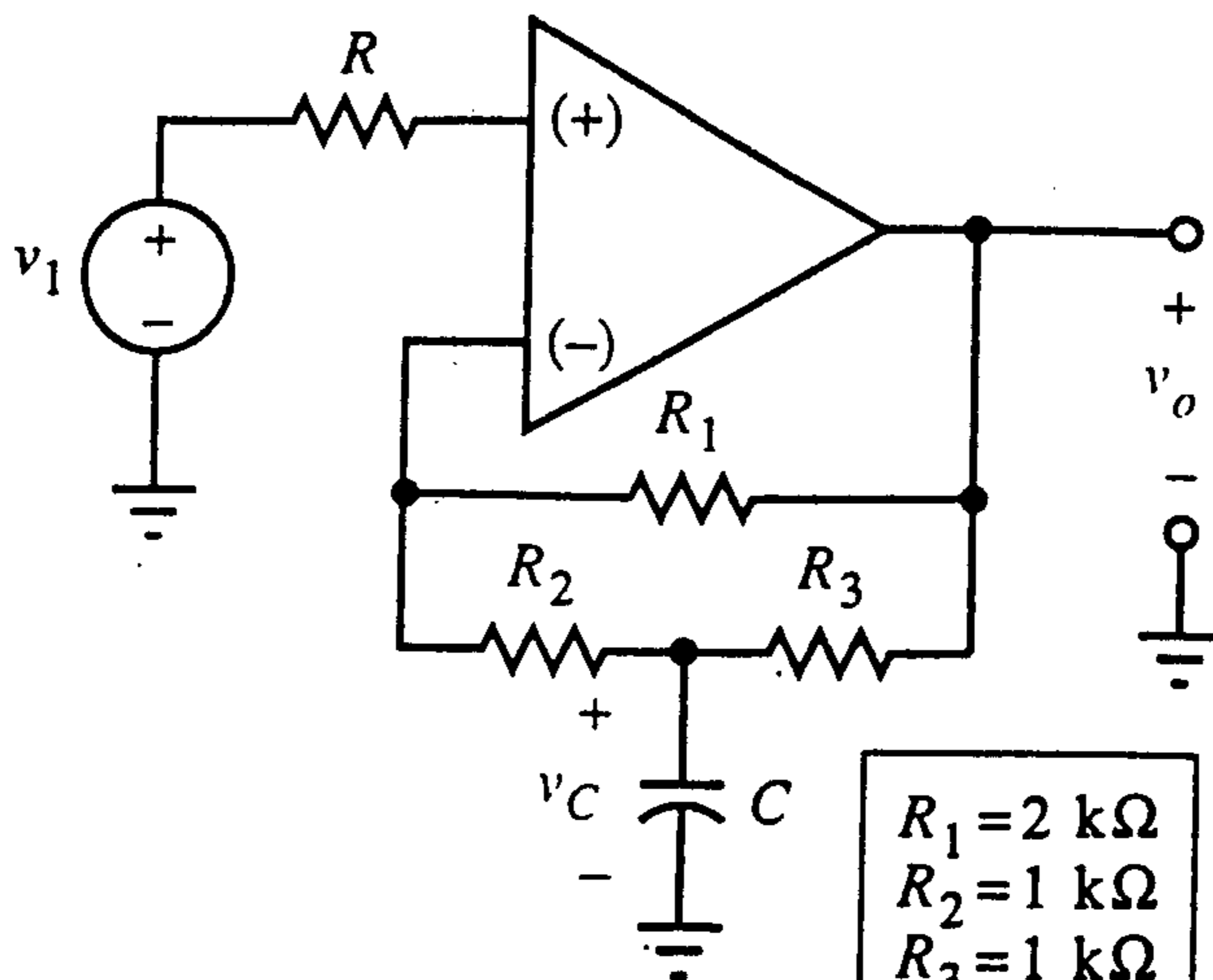- The ideal op-amp circuit shown in Fig.P.2, $v_c(0^-) = 2V$ and $v_1 = 5u(t) V$. Find and sketch $v_o(t)$ for $t \geq 0$. (20 %)



$R_1 = 2 \text{ k}\Omega$
 $R_2 = 1 \text{ k}\Omega$
 $R_3 = 1 \text{ k}\Omega$
 $C = 1 \mu\text{F}$

Fig.P.2



57

國立臺灣科技大學
九十學年度碩士班招生考試試題

系所組別：電機工程系甲組
科目：電路學

3. A 2400-V (line-to-line) three-phase motor is operated at rated voltage and has a mechanical output of 50 horsepower. The motor is operating with an efficiency of 90% and a power factor of 0.8 lagging. (1 hp = 0.746 kW.) Find :
- (1) the complex power absorbed by the motor (5 %)
 - (2) the line current (5 %)
 - (3) the kVAR rating of a lossless three-phase capacitor that must be connected in parallel with the motor to obtain a combined power factor of 0.9 lagging (5 %)
 - (4) the line current required for the combined load (5 %)
4. A series band-pass RLC filter uses a resistance $R=2.2 \text{ k}\Omega$. Let $H(j\omega)$ be the transfer function of the band-pass filter.
- (1) Choose the value of L and C to pass the fifth harmonic of a 10-kHz input triangular wave without attenuation and $|H(j\omega_7)|=1/25$, where ω_7 is the angular frequency of the seventh harmonic. (14 %)
 - (2) Make a rough sketch of the output to illustrate the predominant shape of the output waveform. (6 %)
5. A half-rectified cosine voltage with a peak of 1 V and period 1ms is input to a low-pass RC filter. ($RC=10 \text{ ms}$)
- (1) Give the formula for the n-th complex Fourier coefficient of the output. (12 %)
 - (2) Evaluate your answer to (1) for $n = 0, \pm 1, \pm 2, \pm 3$. (8 %)



58