

國立臺灣科技大學

九十一學年度碩士班招生考試試題

系所組別：電子工程系乙一組、電子工程系乙二組、電子工程系乙三組
 科目：電子電路學

(總分 100 分)

- A BJT operates at 27° with $\beta=250$ in an active region. (We specify $r_{bb}'=0$, $r_o=40\text{K}\Omega$, $C_\mu=3\text{pF}$, and $C_\pi=100\text{pF}$)
 - Plot its high-frequency hybrid- π model, (5%)
 - If the BJT is operated at $I_C=5\text{mA}$, find its transconductance $g_m=?$ (A/V) (3%)
 - From (2), find its input impedance $r_\pi=?$ (3%)
 - Find the unity-gain bandwidth f_T of the BJT in common-emitter configuration when its short-circuit current gain approaches one.
(注意：公式必須先推導出來才給分) (9%)
- A differential amplifier with an active load is shown in Fig. P2a, whose equivalent circuit is shown in Fig. P2b. Find the followings represented by the parameters of the hybrid- π model
 - Output impedance $R_o=?$ (5%)
 - Open-circuit voltage gain $v_o/v_d=?$ (5%)
 - Transconductance $G_m=?$ (5%)
 - Input-impedance $R_i=?$ (5%)
- A RC circuit is shown in Fig. P3. If $v_i(t) = Vu(t)$, find
 - $v_o(t)$, $t \geq 0$; (10%)
 - What is the condition for the $v_o(t)$ being a perfect step-output? (10%)
- An active filter is shown in Fig. P4.
 - Find its transfer function $v_o(t)/v_i(t)=?$ (15%)
 - What kind of this filter is? (5%)
- A transformer-coupled Class-A power amplifier is shown in Fig. P5. We assume that the transformer is ideal and its turns-ratio is $N:1$.
 - Plot the AC and DC load line on i_C - v_{CE} output characteristic curve under producing maximum symmetrical swing.
(注意： i_C - v_{CE} 座標上必須詳細寫出數據才給分) (5%)
 - Find the optimal operating point $Q(I_{CQ}, V_{CEQ})$ for producing maximum symmetrical swing. (5%)
 - Find the maximum average output power $P_{L,ac}=?$ (W) if the input signal is sinusoidal $v_i(t)=V_{im}\sin\omega t$. (5%)
 - Find the maximum power dissipated in the transistor? (5%)
(注意：(2)-(4)題的結果必須以 V_{cc} , R_L 及 N 表示才給分)



國立臺灣科技大學

九十一學年度碩士班招生考試試題

系所組別：電子工程系乙一組、電子工程系乙二組、電子工程系乙三組
 科目：電子電路學

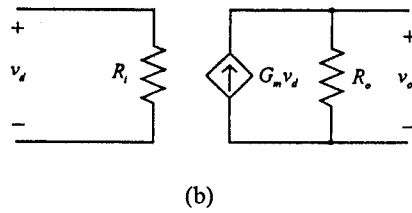
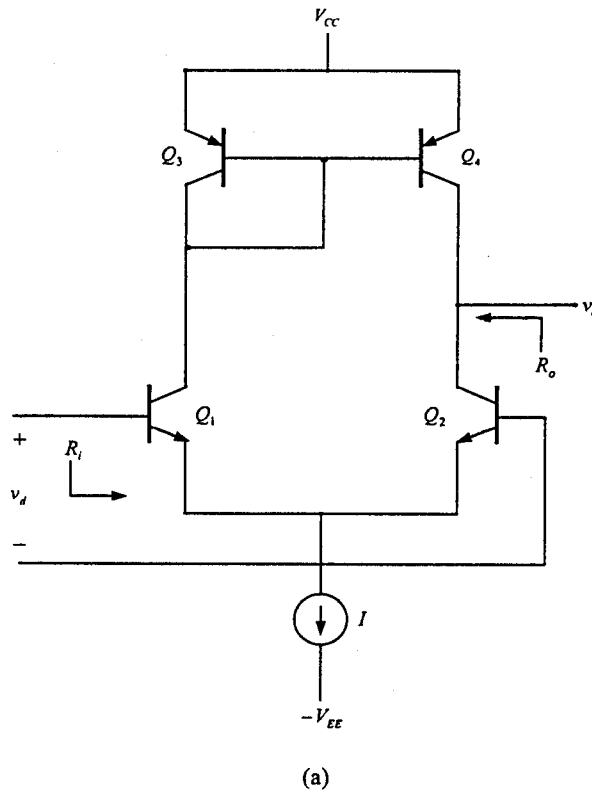


Fig. P2

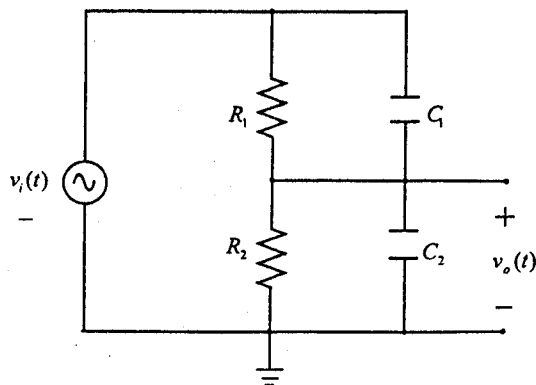


Fig. P3



國立臺灣科技大學
九十一學年度碩士班招生考試試題

系所組別：電子工程系乙一組、電子工程系乙二組、電子工程系乙三組
科目：電子電路學

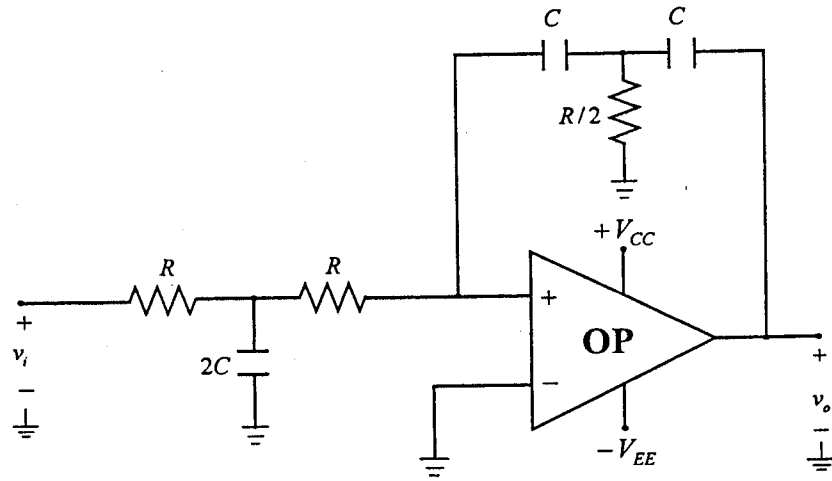


Fig. P4

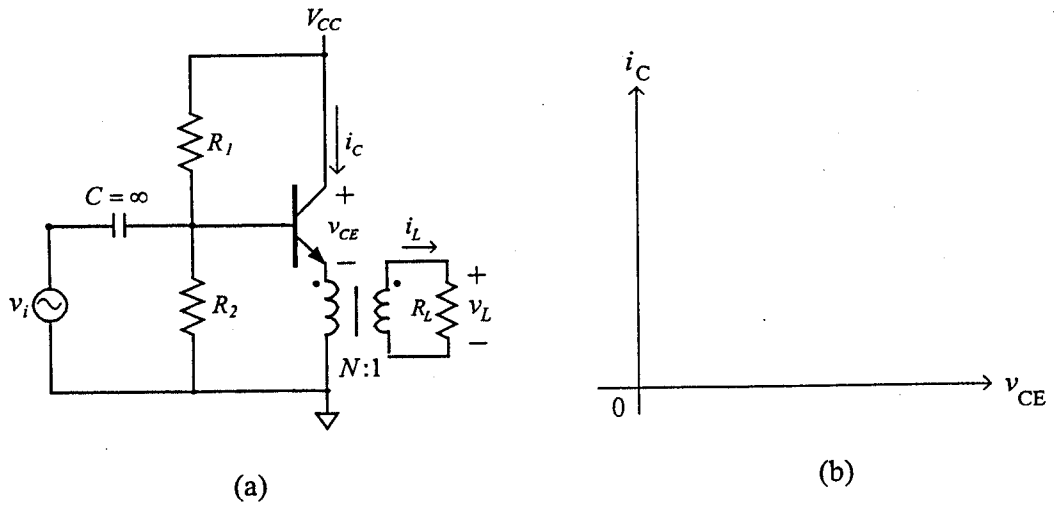


Fig. P5

