
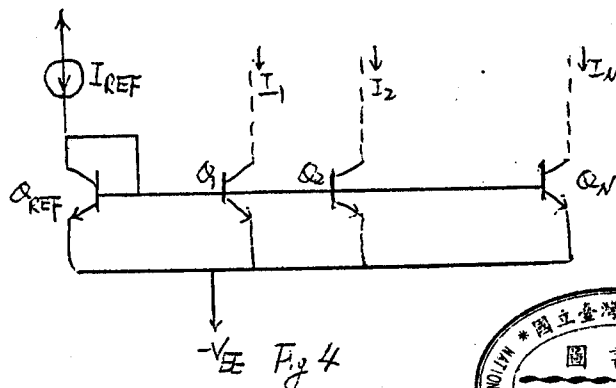
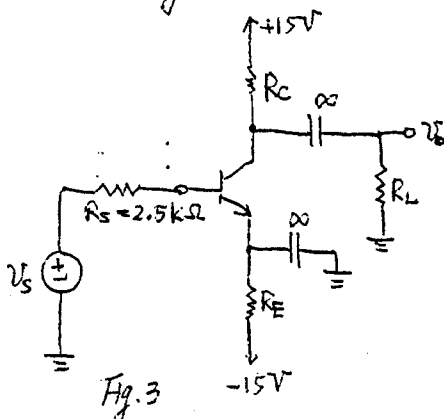
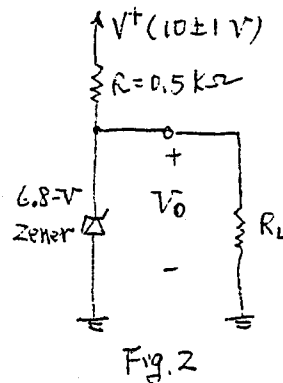


國立臺灣科技大學
九十一學年度碩士班招生考試試題

系所組別：電子工程系丙組
科目：電子學

(總分 100 分)

- (10%) For the circuit shown in Fig. 1 derive an expression for the transfer function V_o/V_i . Find expressions for the magnitude and phase of the response. Note: This circuit functions as a first-order all-pass filter.
- (15%) The 6.8-V zener diode in the circuit of Fig 2 is specified to have $V_z=6.8V$ at $I_z=5mA$, $r_z=20\Omega$, and $I_{zk}=0.2mA$. The supply voltage V^+ is nominally 10V but can vary by $\pm 1V$.
 - Find the change in V_o resulting from the $\pm 1V$ change in V^+ .
 - Find the change in V_o resulting from connecting a load resistance $R_L=2k\Omega$.
 - What is the minimum values of R_L for which the diode still operates in the breakdown region?
- (15%) In the circuit of Fig. 3, v_s is a small sine-wave signal with zero average. The transistor β is 100.
 - Find the value of R_E to establish a dc emitter current of about 1mA.
 - Find R_C to establish a dc collector voltage of about +5V.
 - For $R_L=5k\Omega$ and the transistor $r_o=100k\Omega$, draw the small-signal equivalent circuit of the amplifier and determine its overall voltage gain.
- (10%) Figure 4 shows an N-output current mirror. Assuming all transistors to be matched and have finite β and ignoring the effect of finite output resistances, show that $I_1 = I_2 = \dots = I_N = \frac{I_{REF}}{1 + (N+1)/\beta}$. For $\beta=100$ find the maximum number of outputs for an error not exceeding 10%.

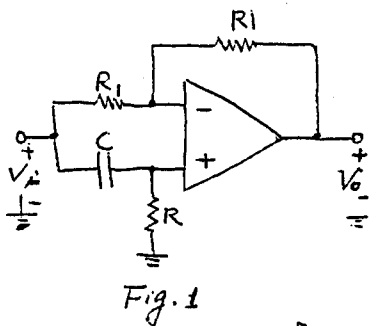

國立臺灣科技大學

九十一學年度碩士班招生考試試題

系所組別：電子工程系丙組

科目：電子學

5. (10%) (1) What is a common-collector amplifier? Please draw an example.
(2) What is a common-emitter amplifier? Please draw an example.
6. (10%) An amplifier has the voltage transfer function $T(s) = \frac{10s}{(1+s/10^2)(1+s/10^5)}$. Find the poles and zeros and sketch the magnitude of the gain versus frequency. Find approximate values for the gain at $\omega = 10, 10^3, \text{ and } 10^6$ rad/s.
7. (10%) Fermi-Dirac probability function : Assume that the Fermi energy level for a particular is 6.25 eV and that the electrons in this material follow the Fermi-Dirac distribution function. Calculate the temperature at which there is a 1 percent probability that a state 0.30eV below the Fermi energy level will not contain an electron.
8. (10%) Consider a three-dimensional infinite potential well. The potential function is given by $V(x) = 0$ for $0 < x < a, 0 < y < a, 0 < z < a$, and $V(x) = \infty$ elsewhere. Start with Schrodinger's wave equation, use the separation of variables technique, and show that the energy is quantized and is given by
- $$E_{n_x, n_y, n_z} = \frac{\hbar^2 \pi^2}{2ma^2} (n_x^2 + n_y^2 + n_z^2)$$
- where $n_x = 1, 2, 3, \dots, n_y = 1, 2, 3, \dots, n_z = 1, 2, 3, \dots$
9. (10%) Consider an n-type silicon semiconductor at $T = 300^\circ\text{K}$ in which $N_d = 10^{16} \text{ cm}^{-3}$ and $N_a = 0$. The intrinsic carrier concentration is assumed to be $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$. Please determine the thermal equilibrium electron and hole concentrations.

