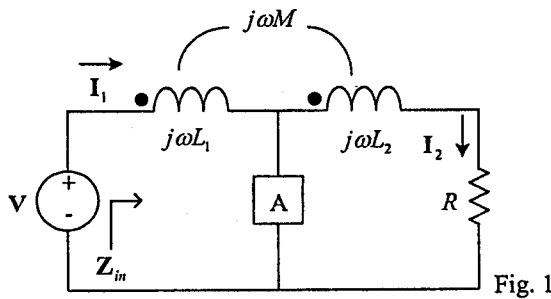


國立臺灣科技大學  
九十一學年度碩士班招生考試試題


系所組別：電機工程系甲組  
科目：電路學

總分 100 分


1. The circuit in Fig. 1 has  $V = 1\angle 0^\circ$  V,  $\omega L_1 = 25\Omega$ ,  $\omega L_2 = 4\Omega$ ,  $\omega M = 10\Omega$  and  $R = 3\Omega$ . (a) Find  $Z_{in}$  and  $I_2/I_1$  when the impedance of element A is  $Z_A = 0\Omega$ . (b) Find  $Z_{in}$  when the impedance of element A is  $Z_A = j5\Omega$ . (20 points)



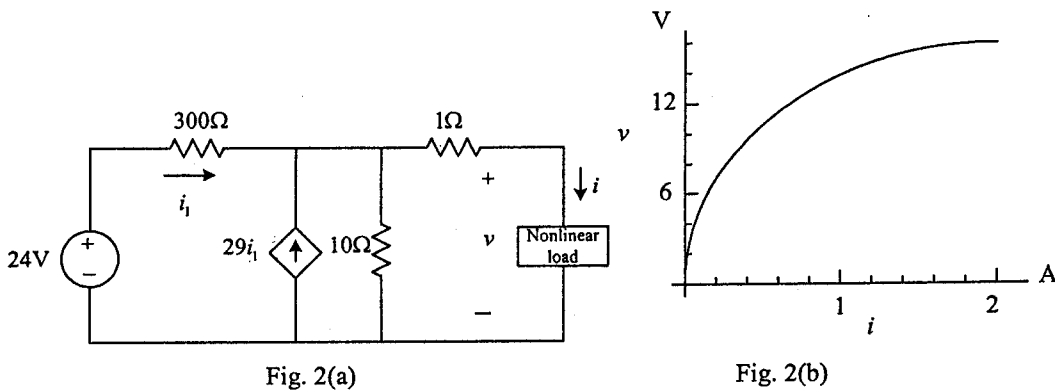2. Fig. 2(a) shows a circuit connected to a nonlinear load. (a) If the V-I characteristic of the nonlinear load is specified as  $v = 3i^2$ , calculate the current  $i$  through the nonlinear load. (b) If the V-I characteristic of the nonlinear load is now specified as the curve shown in Fig. 2(b), determine and show the current  $i$  through the nonlinear load graphically. (20 points)



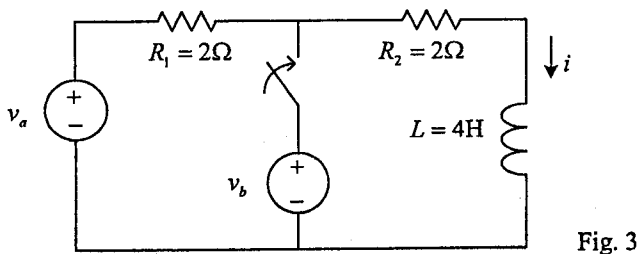3. Fig. 3 shows a first-order circuit with a switch. After having been open for a very long time, the switch is closed at  $t = 0$ . Let  $v_a = 16 \cos(t)$  V and  $v_b = 16$  V. (a) Determine current  $i$  through the inductor for  $t > 0$ . (b) Calculate the average power absorbed by the resistor  $R_2$  when the circuit reaches steady state. (20 points)



國立臺灣科技大學  
九十一學年度碩士班招生考試試題

系所組別：電機工程系甲組  
科目：電路學

4. Two ac networks, A and B, are connected together through two different methods as shown in Fig.4 (a) and (b) respectively. The associated terminal currents and voltages of each connection are as follows :  $I_{ab} = 1\angle 0^\circ$  A and  $V_{aa'} = 2\angle -45^\circ$  V for Fig. 4(a);  $I_{ab'} = 3\angle 0^\circ$  A and  $V_{aa'} = 2\angle 45^\circ$  V for Fig. 4(b). (a) Find  $V_{aa'}$  and  $I_{bb'}$  as indicated in Fig. 4(c). (b) Find  $I_{ab}$  as indicated in Fig. 4(d). (30 points)

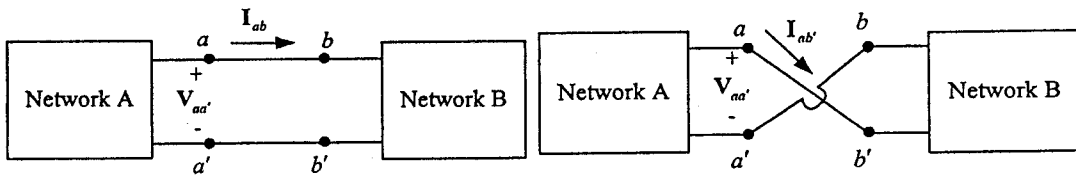


Fig. 4(a)

Fig. 4(b)

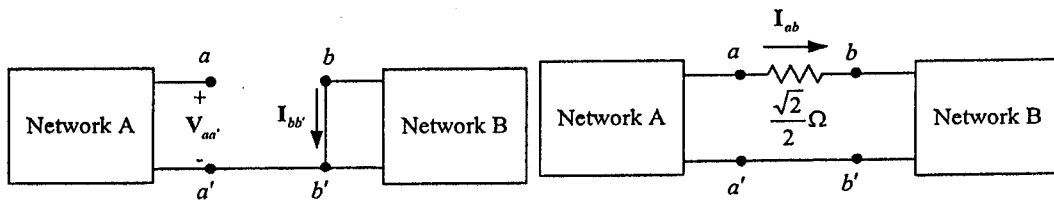


Fig. 4(c)

Fig. 4(d)

5. Fig. 5 shows a difference amplifier using two ideal operational amplifiers. Determine the voltage gain  $v_o / (v_2 - v_1)$  of this difference amplifier. (10 points)

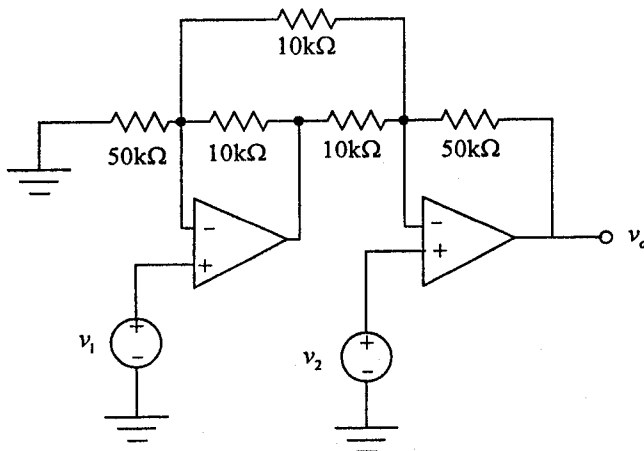


Fig. 5

