

國立臺灣科技大學
九十二學年度碩士班招生考試試題

系所組別：電子工程系碩士班丙組
科 目：電子學

92年

(1) 20% For a three-input ECL (emitter-coupled logic) OR/NOR gate, as shown in figure 1. Assume a drop of 0.7 V between base and emitter of a conducting transistor. (a) Find the logic levels at the output Y (i.e. find $V(0)$ & $V(1)$). (b) Calculate R so that the logic levels at Y' are the complements of those at Y.

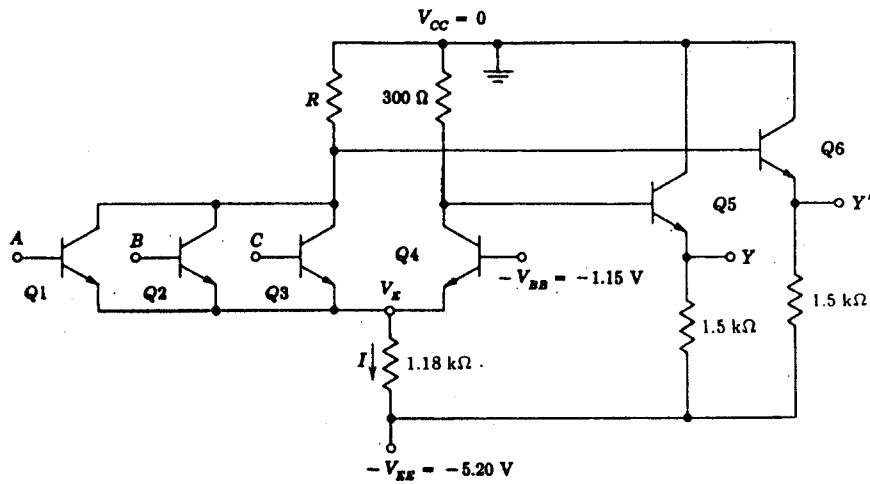


Fig. 1

(2) 15% The small signal low-frequency BJT model is shown in figure 2. For the common-emitter (CE) amplifier shown in figure 3, please find (a) input resistance, (b) voltage gain, (c) voltage gain when $h_{fe}R_e \gg h_{ie}$.

 


Fig. 2

 


Fig. 3

 


Fig. 4

(3) 15% For the common-source amplifier circuit shown in figure 4, please plot the small signal equivalent circuit at high frequency, and explain the meanings of each item.



國立臺灣科技大學

九十二學年度碩士班招生考試試題

系所組別：電子工程系碩士班丙組

科目：電子學

- (4) 10% The electron density of a doped silicon crystal is plotted as a function of temperature, shown in figure 5. Please explain the physical meanings of region A, B, and C, respectively.

 


Fig. 5

- (5) 10% For a typical BJT, please schematically plot the CE current gain (β) as a function of I_c (i.e. $\log(\beta)$ versus I_c), and explain it.
- (6) 10% For a silicon p-n junction, please derive C_j (depletion capacitance per unit area) as a function of ϵ_s (dielectric constant of silicon) and W (depletion width).
- (7) 10% For a typical n-MOSFET, please sketch I_{ds} as a function of V_{ds} for various V_{gs} values with $V_{gs1} > V_{gs2} > V_{gs3} > V_T$, and explain it.
- (8) 10% For a typical MOS capacitor with p-type silicon as the substrate, please sketch the capacitance as a function of applied voltage (i.e. C-V profile) at low frequency (10 Hz) and high frequency (100 kHz), respectively, and explain it.

