

## 國立臺灣科技大學

## 九十二學年度碩士班招生考試試題

系所組別：電機工程系碩士班甲組

科目：電力工程

「總分 100 分」

1. A three-phase Y-connected 220-V (line-to-line), 7.5-kW, 60-Hz, six-pole induction motor has the following parameter values in  $\Omega$ /phase referred to the stator:

$$R_1 = 0.294, R_2 = 0.144, X_1 = 0.503, X_2 = 0.209, X_m = 13.25$$

The total friction, windage, and core losses may be assumed to be constant at 400 W, independent of load. For a slip of 2 percent, compute the stator current, shaft output torque, power factor and efficiency when the motor is operated at rated voltage and frequency. (20%)

2. The following data were obtained for a 50-kVA, 60-Hz, 2400:240-V distribution transformer tested at 60 Hz:

	Voltage, V	Current, A	Power, W
With high-voltage winding open-circuit	240	5.41	186
With low-voltage side short-circuit	48	20.8	617

Determine the efficiency and the voltage regulation at full load, 0.80 power factor lagging. (15%)

3. A 60-Hz, three-phase synchronous motor is observed to have a terminal voltage of 460 V (line-to-line) and a terminal current of 120 A at a power factor of 0.95 lagging. The field-current under this operating condition is 47 A. The machine synchronous reactance is equal to  $1.68 \Omega$ . Assume the armature resistance to be negligible. Calculate the generated voltage  $E_{af}$  (line-to-neutral), the magnitude of the field-to-armature mutual inductance, and the electrical power input to the motor. (15%)

4. In the two-bus system shown in Fig. 1, bus 1 is a slack bus with  $V_1 = 1.0 \angle 0^\circ$  pu. A load of 100 MW and 50 Mvar is taken from bus 2. The line impedance is  $z_{12} = 0.12 + j0.16$  pu on a base of 100MVA.

(a) Determine the bus admittance matrix. (5%)

(b) Substituting for admittances, derive the expression for real and reactive power at bus 2. (5%)

(c) Using Newton-Raphson method, obtain the bus voltage magnitude and phase angle of bus 2. Start with an initial estimate of  $|V_2|^{(0)} = 1.0$  pu and  $\delta_2^{(0)} = 0^\circ$ . Perform one iteration. (10%)

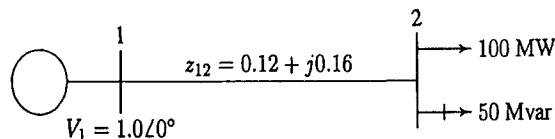


Fig. 1. One-line diagram for Problem 4.



## 國立臺灣科技大學

## 九十二學年度碩士班招生考試試題

系所組別：電機工程系碩士班甲組

科目：電力工程

5. The one-line diagram of a simple power system is shown in Fig. 2. The neutral of each generator is grounded through a current-limiting reactor of 0.25/3 per unit on a 100-MVA base. The system data expressed in per unit on a common 100-MVA base is tabulated below, where the superscripts 1, 2, and 0 are used to represent positive, negative, and zero-sequence quantities, respectively. The generators are running on no-load at their rated voltage and rated frequency with their emfs in phase.
- (a) Find the positive-sequence, negative-sequence, and zero-sequence Thevenin equivalent networks viewed from bus 3 (the faulted bus). (10%)
- (b) Determine the fault current for a single line-to-ground fault at bus 3 through a fault impedance  $Z_f = j0.1$  per unit. (5%)
- (c) Determine the fault current for a line-to-line fault at bus 3 through a fault impedance  $Z_f = j0.1$  per unit. (5%)

Item	Base MVA	Voltage Rating	$X^1$	$X^2$	$X^0$
$G_1$	100	20 kV	0.15	0.15	0.05
$G_2$	100	20 kV	0.15	0.15	0.05
$T_1$	100	20/220 kV	0.10	0.10	0.10
$T_2$	100	20/220 kV	0.10	0.10	0.10
$L_{12}$	100	220 kV	0.125	0.125	0.30
$L_{13}$	100	220 kV	0.15	0.15	0.35
$L_{23}$	100	220 kV	0.25	0.25	0.7125

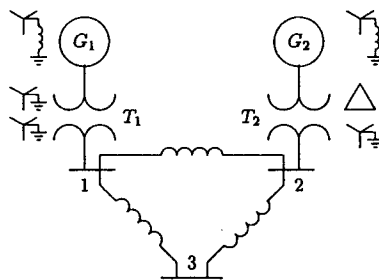


Fig. 2. One-line diagram for Problem 5.

6. The fuel-cost functions in \$/h for three thermal plants are given by
- $$C_1 = 350 + 7.20P_1 + 0.0040P_1^2$$
- $$C_2 = 500 + 7.30P_2 + 0.0025P_2^2$$
- $$C_3 = 600 + 6.74P_3 + 0.0030P_3^2$$
- where  $P_1$ ,  $P_2$ , and  $P_3$  are in MW. Neglecting line losses and generator limits, determine the optimal scheduling of generation for  $P_D = 450$  MW. (10%)

