

國立臺灣科技大學

九十二學年度碩士班招生考試試題

系所組別：電機工程系碩士班乙二組、電機工程系碩士班丙二組

科目：電子學

總分 100 分

1. Consider the following MOSFET common-source stage:

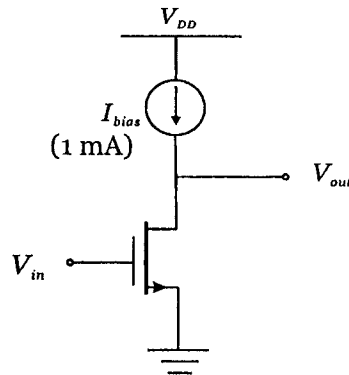


Fig. P1.1

with $V_{DD} = 5$ V, $I_{bias} = 1$ mA. For the MOSFET, assume the threshold voltage, V_{TN} , is 0.7 V, the process transconductance parameter, k'_n , is $100 \mu\text{A}/\text{V}^2$, the channel-length modulation, λ_n , is 0.05 V^{-1} , and the body-effect coefficient is neglected.

- (5 points) Find the dc value of the input voltage such that the ac voltage gain is -100 .
- (5 points) Find the value of $(W/L)_n$ of this NMOS transistor.
- (10 points) If the circuit is reconfigured as shown in Fig. P1.2 and assume that the current source is actually implemented by a PMOS circuit where the PMOS has $V_{TP} = -0.7$ V, $k'_p = 30 \mu\text{A}/\text{V}^2$, $(W/L)_p = 10$, $\lambda_p = 0.03 \text{ V}^{-1}$. Find the new ac voltage gain and voltage V_{GP} , respectively.

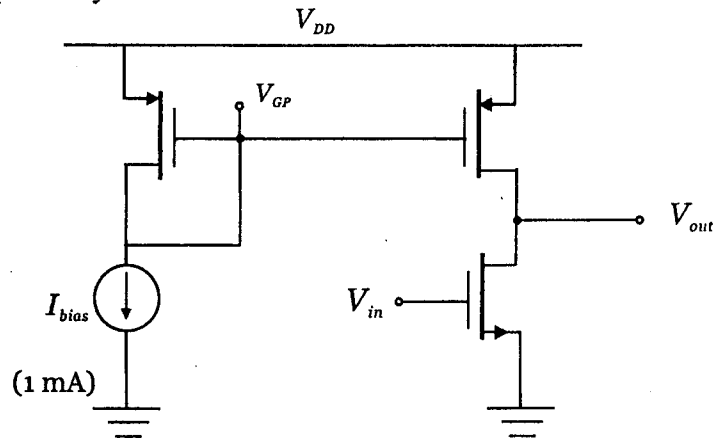


Fig. P1.2



國立臺灣科技大學

九十二學年度碩士班招生考試試題

系所組別：電機工程系碩士班乙二組、電機工程系碩士班丙二組

科目：電子學

2. The following figure, Fig. P2, is considered.

- (a) (10 points) Determine the Q-point values I_{CQ} and V_{CEQ} of this transistor circuit.
- (b) (10 points) Sketch the ac equivalent circuit under the assumption that the output capacitor represents a short circuit for ac frequencies of interest and find an expression for the ac current gain $A_I = \frac{I_{out}}{I_{in}}$.

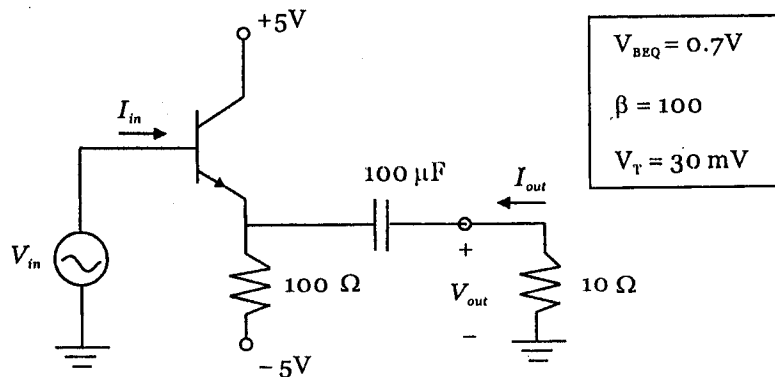


Fig. P2

3. (10 points) Assuming the diodes in the circuits of Fig. P3 are ideal, find the values of the labeled voltage V_x and current I .

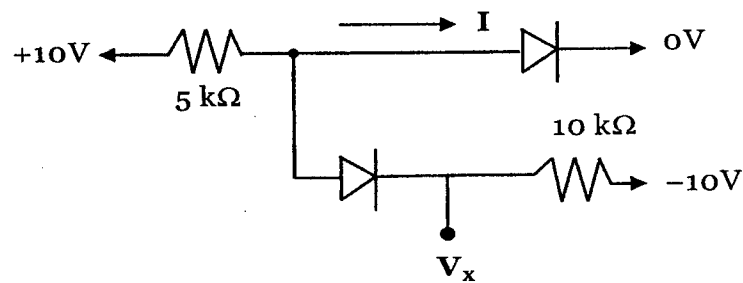


Fig. P3

4. (18 points) Consider the circuit shown in Fig.P4. Let $R_S = 100K\Omega$, $R_E = 820\Omega$, $r_x = 1.1K\Omega$, Q_2 be biased at $I_E = 5mA$, and $\beta_1 = \beta_2 = 100$ for Q_1 and Q_2 . Determine R_m , R_{out} , $A_v = \frac{V_o}{V_s}$ and $A_I = \frac{I_{E2}}{I_s}$. Calculate to 3 significant digits.



國立臺灣科技大學

九十二學年度碩士班招生考試試題

系所組別：電機工程系碩士班乙二組、電機工程系碩士班丙二組

科目：電子學

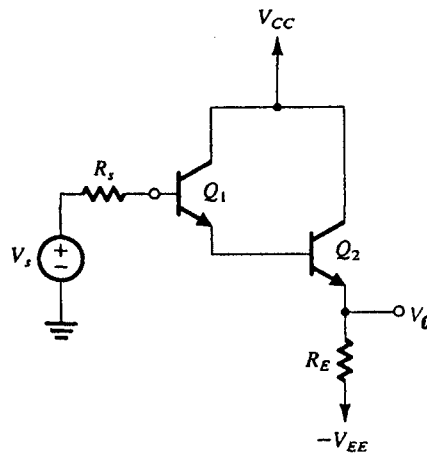


Fig. P4

5. (16 points) For the circuit shown in Fig.P5, describe the theory of operation of the circuit by drawing a diagram in which the voltage transfer curve, the v_i vs. t and the v_o vs. t curves are put together and the input signal is a sinusoid. Determine the power conversion efficiency η and the maximum efficiency η_{\max} .


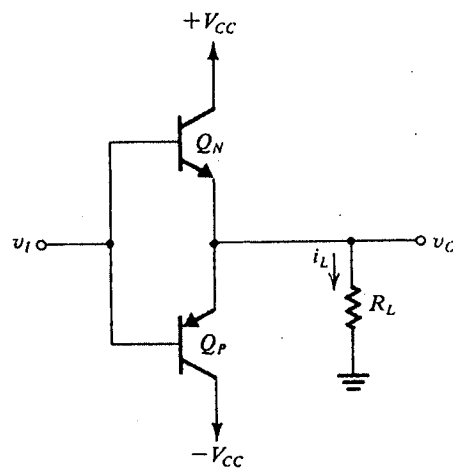


Fig. P5

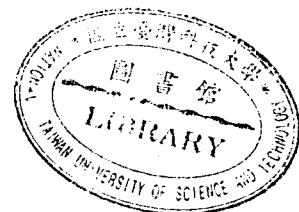

國立臺灣科技大學
九十二學年度碩士班招生考試試題

系所組別：電機工程系碩士班乙二組、電機工程系碩士班丙二組
科 目：電子學

6. (16 point) Derive the equation for calculating the output voltage V_o given the input voltage V_i for the circuit shown in Fig.P6. Draw the Bode diagram for the voltage transfer characteristic and mark the important values on the diagram.

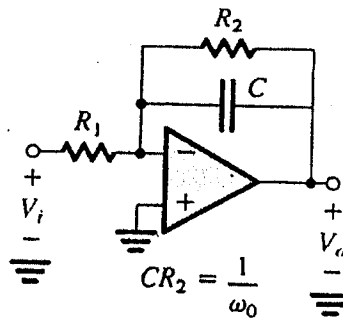


Fig.P6

