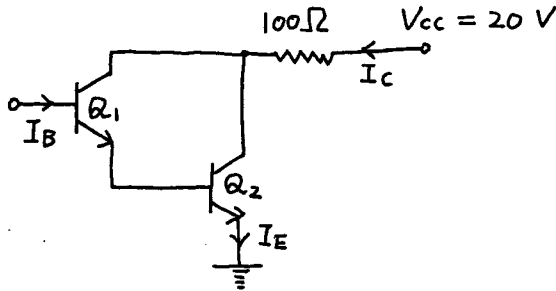


國立臺灣科技大學
九十三學年度碩士班考試試題


系所組別：電子工程系丙組
科目：電子學

總分 100 分


- (1) 10% For the circuit shown, α_1 (common base current gain)=0.99, $\alpha_2=0.98$, $I_E=120$ mA. Please calculate I_C/I_B .



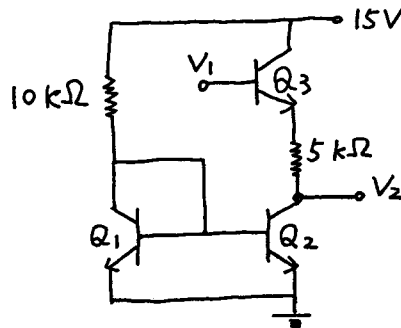
- (2) 10% For the level-shift network shown, calculate $V_2 - V_1$. Assume identical transistors with very large β values.



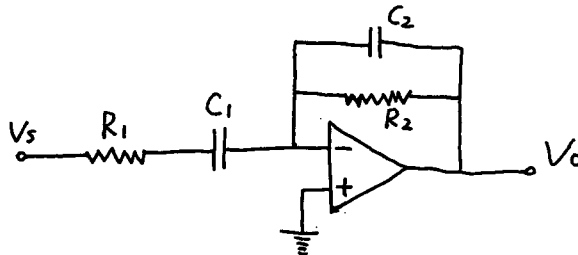- (3) 15% Find the transfer function for the OP AMP configuration shown.



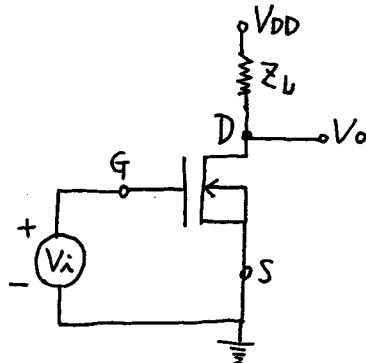- (4) 15% Please plot the small-signal equivalent circuit at high frequency, for the common source amplifier circuit.



國立臺灣科技大學
九十三學年度碩士班考試試題

系所組別：電子工程系丙組
科 目：電子學

- (5) 10% Please sketch I_{DS} as a function of V_{DS} , for a typical n-MOSFET at a proper gate bias, and explain why.
- (6) 10% Please qualitatively explain the "Compton effect".
- (7) 15% Please sketch the typical forward current-voltage characteristics (current shown in Log scale) for a Si pn junction diode, and explain why. (*at low, medium, high current level*)
- (8) 15% Please sketch the electrical resistivity as a function of temperature for metal, superconductor, and intrinsic semiconductor, respectively, and explain why.

