

國立臺灣科技大學
九十三學年度碩士班考試試題

系所組別：電機工程系乙二組、電機工程系丙二組
科目：電子學

1. For the circuit shown in Fig. P1, 總分 100 分
- (a) Express v_o as a function of v_1 and v_2 . (5%)
 - (b) What is the input resistance seen by a source connected between the two input terminals (differential mode)? (5%)
 - (c) What is the input resistance seen by a source connected to both input terminals simultaneously (common mode)? (5%)

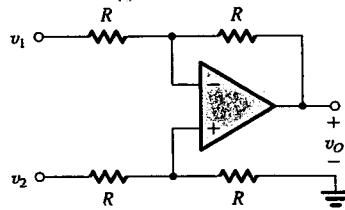


Fig. P1

2. For the circuit shown in Fig. P2, find V_B and V_E for $v_i = +5V, -3V, -10V$, respectively. The BJTs have $\beta = 100$. (15%)

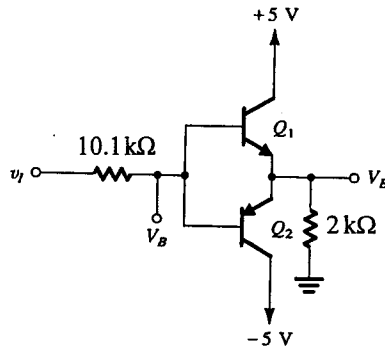


Fig. P2

3. Consider the circuit shown in Fig. P3 with two identical depletion-type MOSFETs ($I_{DSS} = 4mA$ and $|V_t| = 2V$) and three resistors. The function of Q_1 and R_1 is to establish the bias current for Q_2 . It is known that Q_1 operates in saturation region when $v_i = 0V$.
- (a) What is the value of $k'_n W/L$ for these transistors? (3%)
 - (b) For $R_3 = 4k\Omega$ and $R_1 = R_2$, determine the value of R_1 so that $I_{D1} = I_{D2} = 1mA$. (5%)
 - (c) Draw the $v_o - v_i$ characteristics while v_i varies from $-1V$ to $+1V$. (5%)
 - (d) Give a suitable name for this circuit. (3%)

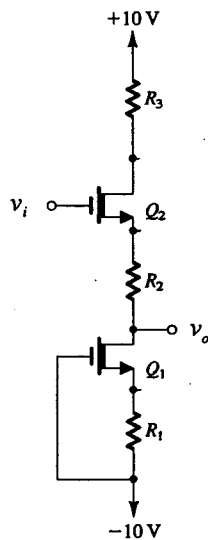


Fig. P3



國立臺灣科技大學

九十三年學年度碩士班考試試題

系所組別：電機工程系乙二組、電機工程系丙二組

科 目：電子學

4. Consider the BiCMOS amplifier shown in Fig. P4. The BJT has $|V_{BE}| = 0.7\text{V}$, $\beta = 200$, $C_{\mu} = 0.8\text{pF}$ and $f_T = 600\text{MHz}$. The NMOS transistor has $V_t = 1\text{V}$, $k'_n W/L = 2\text{mA/V}^2$, and $C_{gs} = C_{gd} = 1\text{pF}$. After dc analyzing, the bias currents of Q_1 and Q_2 are $I_{D1} = 0.1\text{mA}$ and $I_{C2} = 1\text{mA}$, respectively.
- Calculate the small-signal parameters g_{m1} , g_{m2} and $r_{\pi 2}$ of Q_1 and Q_2 . (6%)
 - Determine the overall voltage gain V_o/V_s of the amplifier at midband frequencies. (5%)
 - Evaluate $C_{\pi 2}$ of Q_2 . (3%)
 - Estimate the higher 3-dB frequency f_H of this amplifier. (5%)

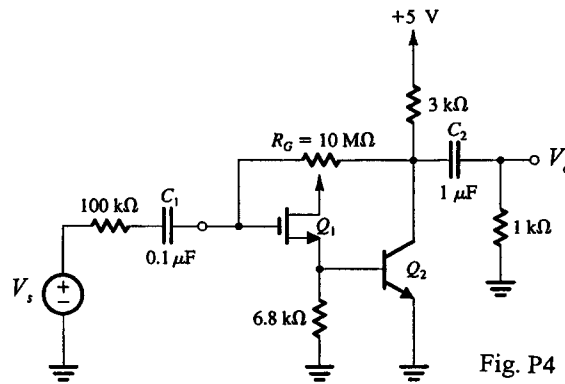


Fig. P4

5. A bridge amplifier configuration with high input resistance is shown in Fig. P5. Find the gain v_o/v_i . (15%)

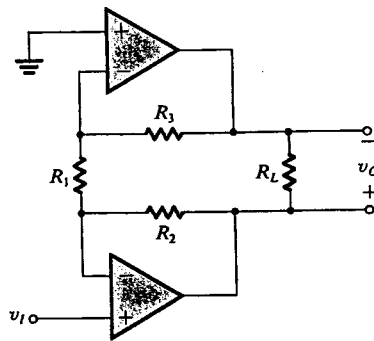


Fig. P5

6. A voltage signal source with a resistance $R_s = 10\text{k}\Omega$ is connected to the input of a common-emitter BJT amplifier. Between base and emitter is connected a tuned circuit with $L = 1\mu\text{H}$ and $C = 200\text{pF}$. The transistor is biased at 1mA and has $\beta = 200$, $C_{\pi} = 10\text{pF}$ (emitter-base capacitance) and $C_{\mu} = 1\text{pF}$ (collector-base capacitance). The transistor load is a resistance of $5\text{k}\Omega$. Find the Q factor and the center-frequency gain of this single-tuned amplifier. (20%)

