

國立臺灣科技大學
九十四學年度碩士班招生考試試題

系所組別：電子工程系碩士班乙一組、乙二組、乙三組
科 目：電子學

總分 100 分

1. Consider the complementary BJT class B output stage as shown in Fig. P1 and neglect the effects of V_{BE} and V_{CEsat} . For $\pm 10\text{-V}$ power supplies and a $100\text{-}\Omega$ load resistance, (1) what is the maximum sine-wave output power available $P_{L,max}$? (2) What is the power conversion efficiency η_1 ? For output signals of half this amplitude ($V_{o,max}/2$), (3) find the output power P_L , (4) the supply power P_{CC} , and (5) the power conversion efficiency η_2 ? (20%)

 


Fig. 1

2. For the circuit shown in Fig. P2, (1) find g_{m1} , g_{m2} , and the mid-band gain A_M ? and (2) the upper 3-dB frequency $f_H = f_{-3dB}$? For the BJT, $\beta = 200$, $C_\mu = 0.8\text{pF}$, and $f_T = 600\text{MHz}$. For the NMOS, $V_t = 1\text{V}$, $k'W/L = 2\text{mA/V}^2$, and $C_{gs} = C_{gd} = 1\text{pF}$. (3) Find C ? for a low cutoff of 10Hz . (20%)

 


Fig. P2

92



國立臺灣科技大學

九十四學年度碩士班招生考試試題

系所組別：電子工程系碩士班乙一組、乙二組、乙三組

科目：電子學

3. For the two-terminal circuit of Fig. P3, known as the V_{BE} -multiplier, assume I to be a sufficiently large and β to be very high and find expressions for (1) the dc voltage drop $V_x=?$ and (2) the incremental resistance $r_x=?$ between X and ground. (3) find the values of $V_x=?$ and $r_x=?$ for $R_1=R_2=1\text{ k}\Omega$, $I=10\text{mA}$, and $V_{BE}=0.7\text{V}$. (10%)

 


Fig. P3

93



國立臺灣科技大學
九十四學年度碩士班招生考試試題

系所組別：電子工程系碩士班乙一組、乙二組、乙三組
科 目：電子學

4. (15%) For the circuit shown in Fig. 1, deduce the voltage gain v_o/v_{id} . Assume ideal OPAMP is used.

 


Fig. 1

5. (20%) Refer to the circuit in Fig. 2 where the output resistance of current source I is R_{SS} :

- (a) Let the two drain resistors be denoted R_{D1} and R_{D2} where $R_{D1} = R_D + \Delta R_D/2$ and $R_{D2} = R_D - \Delta R_D/2$ ($\Delta R_D \ll R_D$). Also let $g_{m1} = g_m + \Delta g_m/2$ and $g_{m2} = g_m - \Delta g_m/2$ ($\Delta g_m \ll g_m$) where g_{m1} and g_{m2} are the transconductances of Q_1 and Q_2 respectively. Please find the CMRR of the circuit in Fig. 2.
- (b) If the bias current I is increased with R_{SS} , $\Delta g_m/g_m$, $\Delta R_D/R_D$, and other circuit parameters unchanged, will the CMRR be increased, decreased, or kept the same? Deduce or explain your answer.

 


Fig. 2



國立臺灣科技大學
九十四學年度碩士班招生考試試題

系所組別：電子工程系碩士班乙一組、乙二組、乙三組
科 目：電子學

- 6 . (15%) The amplifier in the feedback system shown Fig. 3(a) has an open loop gain A with amplitude and phase shown in Fig. 3(b):
- (a) Is the open-loop amplifier with gain A stable? How many poles and zeroes does it have?
 - (b) If the feedback system is required to have a 45° phase margin for its closed-loop gain, then $\beta = ?$ Assume β is frequency-independent.

 


Fig. 3(a)

 


Fig. 3(b)



95