

國立臺灣科技大學

九十四學年度碩士班招生考試試題

系所組別：電子工程系碩士班乙二組

科目：電路學

總分 100 分

1. The circled numbers in Figure 1 are node numbers. The node voltages of this circuit are $v_1=5V$, $v_2=7V$, and $v_3=6V$. Determine
- The value of the current i_b . (10%)
 - The value of the gain r . (10%)

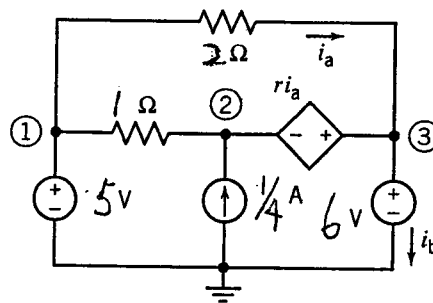


Figure 1

2. Find the Thévenin equivalent circuit for the circuit shown in Figure 2 (10%)

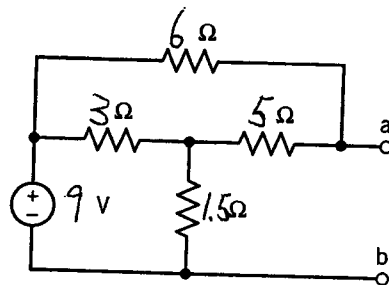


Figure 2

99



國立臺灣科技大學
九十四學年度碩士班招生考試試題

系所組別：電子工程系碩士班乙二組
科 目：電路學

3. Find $v_c(0^+)$ and $dv_c(0^+)/dt$ if $v_c(0^-)=30V$ for the circuit of Figure 3 (10%)

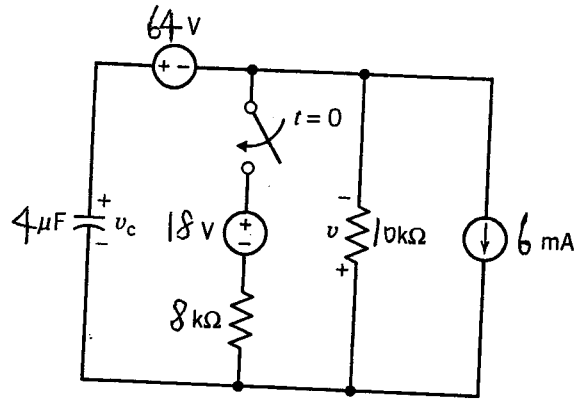


Figure 3

4. The circuit shown in Figure 4 is at steady state before the switch closes at $t=0$. The switch remains closed for 2 sec and then opens. Determine the inductor current. (10%)

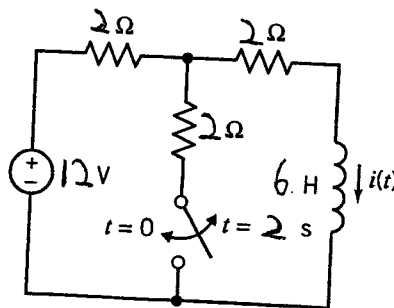


Figure 4 100



國立臺灣科技大學

九十四學年度碩士班招生考試試題

系所組別：電子工程系碩士班乙二組

科目：電路學

5. The circuit shown in Fig. 1 is excited by two sources, where $v_s(t) = 10 \cos(2t)$ and $i_s(t) = 5 \cos(t + 45^\circ)$.

- (a) Calculate $v_R(t)$, the voltage across the $1\text{-}\Omega$ resistor. (5 %)
 (b) Find the average power dissipated in the $1\text{-}\Omega$ resistor. (5 %)
 (c) Find the average power supplied by the 1-H inductor. (5 %)

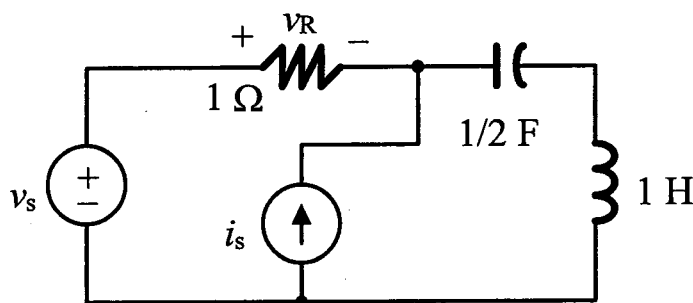


Fig. 5

6. For the rms phasor circuit shown in Fig. 2, Z_L is the load impedance.

- (a) Convert all but the load impedance to its Thevenin equivalent circuit. (4 %)
 (b) For the maximum power transfer, determine Z_L . (2 %)
 (c) Continued from (b), calculate the maximum power drawn by Z_L . (4 %)

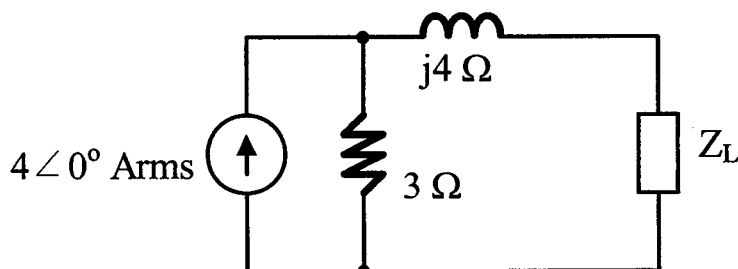


Fig. 6

7. For the phasor circuit shown in Fig. 3, $Z_L = R_L + jX_L$ is the load impedance, and $Z_C = jX_C$ is the compensating impedance for power factor correction. If the desired total power factor

is to be 1, please prove that $X_C = \frac{R_L^2 + X_L^2}{-X_L}$. (10 %)

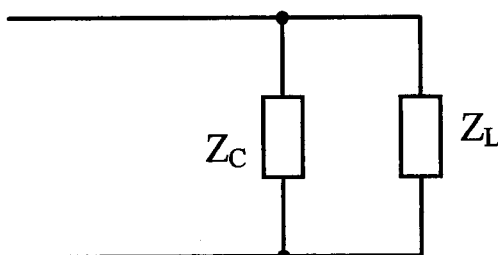


Fig. 7



101

國立臺灣科技大學

九十四學年度碩士班招生考試試題

系所組別：電子工程系碩士班乙二組

科 目：電路學

8. For the circuit shown in Fig. 4, $v_s(t) = 12[1 + u(t)]$ V, where $u(t)$ is the unit step function. Assuming that the steady-state has been reached long before $t = 0$,
- (a) Calculate $i_L(0^-)$ and $v_C(0^-)$. (5 %)
- (b) Find $v_C(t)$ for $t > 0$. (10 %)

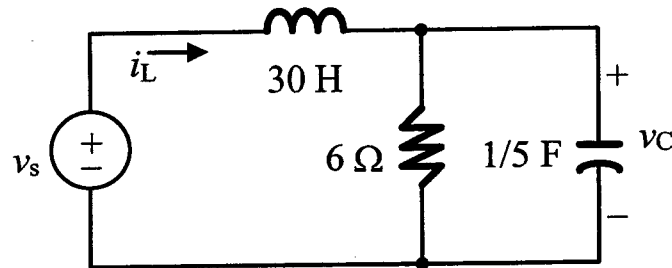


Fig. 8

102

