

國立臺灣科技大學  
九十四學年度碩士班招生考試試題

系所組別：電機工程系碩士班乙二組、電機工程系碩士班丙二組  
科 目：電子學

總分 100 分

1. Consider a peak rectifier fed by a 60-Hz sinusoid having a peak value  $V_p=160\text{V}$ , as shown in Figure 1. Let the load resistance  $R = 16\text{k}\Omega$ .
  - (a) Find the value of the capacitance  $C$  that will result in a peak-to-peak ripple of 5V. (10%)
  - (b) Draw approximately the voltage waveforms  $v_i$  and  $v_o$  in the peak rectifier circuit. (10%)

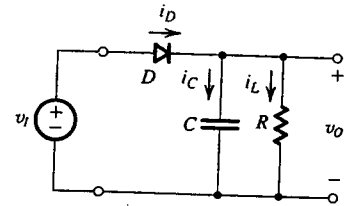


Figure 1

2. (a) Design the circuit shown in Figure 2 so that the transistor operates in saturation with  $I_D = 0.5\text{ mA}$  and  $V_D = +3\text{V}$ . Let the enhancement-type PMOS transistor have  $V_t = -1\text{ V}$  and  $k'_p(W/L) = 1\text{ mA/V}^2$ . Neglect the channel-length modulation effect. (15%)
- (b) What is the largest value that  $R_D$  can have while maintaining saturation-region operation? (5%)

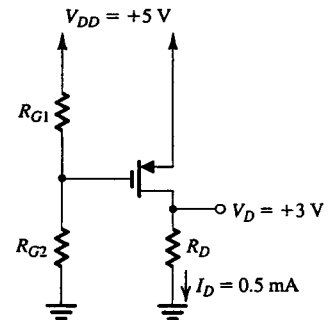


Figure 2

131



國立臺灣科技大學

九十四學年度碩士班招生考試試題

系所組別：電機工程系碩士班乙二組、電機工程系碩士班丙二組  
 科目：電子學

Problem 3:

For the following circuit that uses shunt-series feedback.

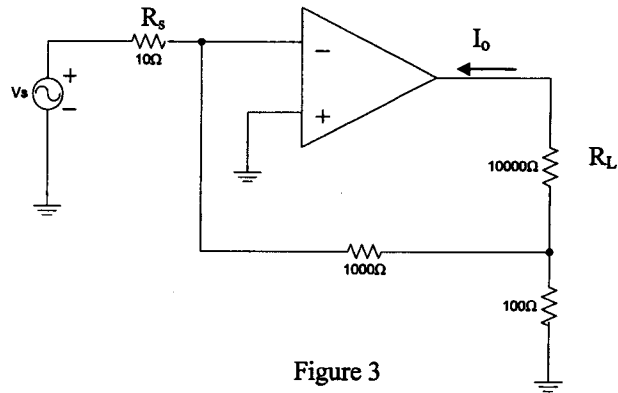


Figure 3

- (a) Find the closed loop gain  $I_o / I_s$ . (10%)  
 (b) The input resistance  $R_{in}$  (not including  $R_s$ ). (5%)  
 (c) The output resistance  $R_{out}$  (not including  $R_L$ ). (5%)

For the op-amp plotted in Figure 3, some available parameters are listed below:

1. Open loop voltage gain of 10,000 V
2. Differential input resistance = 100,000  $\Omega$
3. Output resistance = 1000  $\Omega$

132



國立臺灣科技大學  
九十四學年度碩士班招生考試試題

系所組別：電機工程系碩士班乙二組、電機工程系碩士班丙二組  
科 目：電子學

Problem 4:

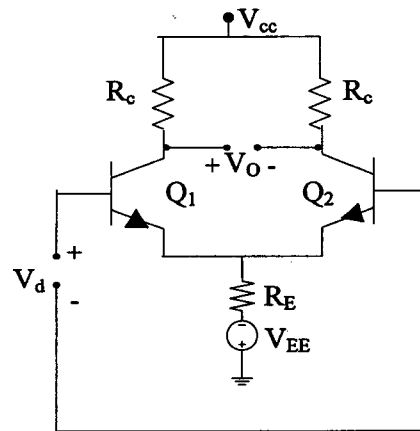


Figure 4

Some available parameters are listed below:

1.  $Q_1 = Q_2$
  2.  $V_{CC} = 15 \text{ V}$
  3.  $V_T = 0.026 \text{ V}$
  4.  $V_A = 80 \text{ V}$
  5.  $\beta = 400$
  6.  $R_C = 20 \text{ k}\Omega$
  7.  $R_E = 28.6 \text{ k}\Omega$
- ( $1 \text{ k} = 1000$ )

Using half circuit models to find out

- (a) The differential gain  $A_d$  (5%)
- (b) The common-node gain  $A_{cm}$  (5%)

133



國立臺灣科技大學

九十四學年度碩士班招生考試試題

系所組別：電機工程系碩士班乙二組、電機工程系碩士班丙二組  
 科目：電子學

5. We wish to analyze the transistor amplifier shown in Figure 5 to determine its voltage gain for small signal operation. Please answer the following questions:
- (a) Determine the small signal parameters of  $r_e$ ,  $g_m$  and  $r_x$ . (10%)
- (b) Determine the voltage gain  $A_v = v_o/v_i$ . (10%)

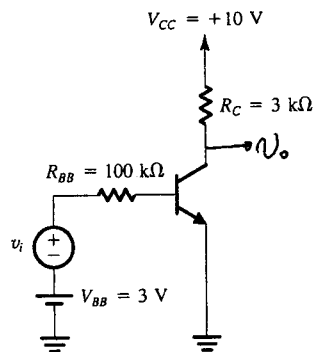


Figure 5

6. Figure 6 shows an ideal voltage amplifier having a gain of  $-100\text{V/V}$  with an impedance  $Z$  of  $1\text{-pF}$  capacitance connected between its output and input terminals.
- (a) Draw the equivalent Miller equivalent circuit. (5%)
- (b) Derive the transfer function of  $V_o(s)/V_{sig}(s)$ . (5%)

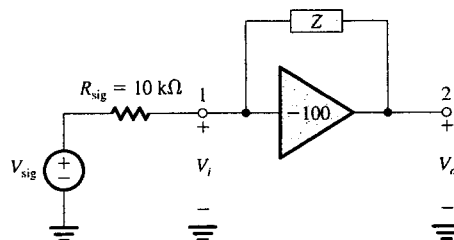


Figure 6

134

