

## 國立台灣科技大學九十五學年度碩士班招生試題

系所組別：電子工程系碩士班乙一組、乙二組、乙三組

科目：電子學

總分 100 分

1. For the transistor in the circuit in Fig. 1, the parameters are  $\beta=100$  and  $V_A=\infty$ . (a) Find the quiescent values of  $I_{CQ}$  and  $V_{CEQ}$ . (b) Find the small-signal parameters  $g_m$ ,  $r_{\pi}$ , and  $r_o$ . (c) Find the input resistances  $R_{ib}$  and  $R_{is}$ . (d) Find the small-signal voltage gain  $A_v=v_o/v_s$  and the small-signal current gain  $A_i=i_o/i_s$ . ( $V_{BE(on)}=0.7V$ ,  $V_T=0.026V$ . Assume the capacitors  $C_{C1}$  and  $C_{C2}$  are shorted out for small signal. Also, only  $g_m$ ,  $r_{\pi}$ , and  $r_o$  are used in the small-signal model of the BJT.) (20%)

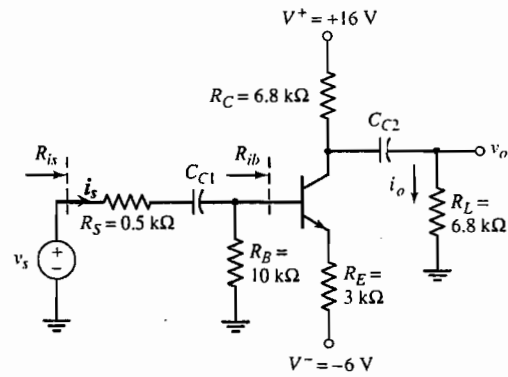


Fig. 1

2. The transistor in the source-follower circuit in Fig. 2 has parameters  $K_p=2mA/V^2$ ,  $V_{TP}=-2V$ , and  $\lambda=0.02V^{-1}$ . The circuit parameters are  $R_L=4k\Omega$ ,  $R_S=4k\Omega$ ,  $R_1=1.24M\Omega$ , and  $R_2=396k\Omega$ . (a) Calculate the quiescent values of  $I_{DQ}$ ,  $V_{SDQ}$  and the small-signal parameters  $g_m$ ,  $r_o$ . (b) Determine the small-signal voltage gain  $A_v=v_o/v_s$  and the small-signal current gain  $A_i=i_o/i_s$ . (c) Calculate the output resistance  $R_o$ . (Assume the capacitors  $C_{C1}$  and  $C_{C2}$  are shorted out for small signal. Also, only  $g_m$  and  $r_o$  are used in the small-signal model of the MOSFET.) (15%)

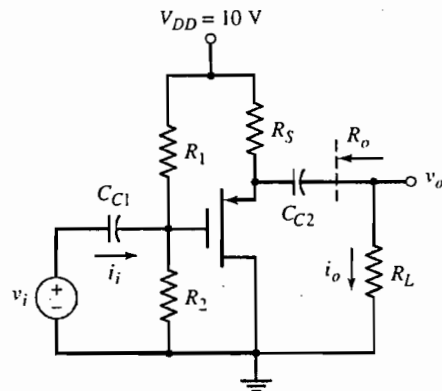


Fig. 2

88



## 國立台灣科技大學九十五學年度碩士班招生試題

系所組別：電子工程系碩士班乙一組、乙二組、乙三組

科目：電子學

3. In the common-base circuit shown in Fig. 3, the transistor parameters are  $\beta=100$ ,  $V_{BE(on)}=0.7V$ ,  $V_T=0.026V$ , and  $V_A=\infty$ ,  $C_{\pi}=10pF$ , and  $C_{\mu}=1pF$ . (a) Determine the upper 3dB frequencies corresponding to the input and output portions of the equivalent circuit. (b) Calculate the small-signal midband voltage gain. (c) If a load capacitor  $C_L=15pF$  is connected between the output and ground, determine if the upper 3dB frequency will be dominated by the  $C_L$  load capacitor or by the transistor characteristics. (Assume the capacitors  $C_{C1}$ ,  $C_{C2}$  and  $C_B$  are shorted out for small signal. Also, only  $g_m$ ,  $r_{\pi}$ ,  $r_o$ ,  $C_{\pi}$ , and  $C_{\mu}$  are used in the small-signal model of the BJT.) (15%)

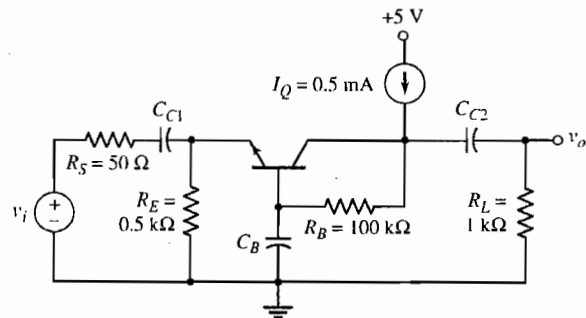


Fig. 3



國立台灣科技大學九十五學年度碩士班招生試題

系所組別： 電子工程系碩士班乙一組、乙二組、乙三組  
 科 目： 電子學

4. Figure 4 shows a simple GaAs MESFET amplifier, with the  $W$  values of the transistors indicated. Assume that the dc component of  $v_i$ , that is  $V_{GS1}$ , biases  $Q_1$  at the current provided by the current source  $Q_2$  so that both devices operate in saturation and that the dc output is at half of the supply voltage. Find:

- (a) the  $\beta$  values for  $Q_1$  and  $Q_2$ ;
- (b)  $V_{GS1}$ ;
- (c)  $g_{m1}$ ,  $r_{o1}$ , and  $r_{o2}$ ; and
- (d) the small-signal voltage gain. (20%)

TYPICAL PARAMETER VALUES FOR  
 GaAs MESFETS AND SCHOTTKY DIODES  
 IN  $L = 1 \mu\text{m}$  TECHNOLOGY,  
 NORMALIZED FOR  $W = 1 \mu\text{m}$

$V_t = -1.0 \text{ V}$   
 $\beta = 10^{-4} \text{ A/V}^2$   
 $\lambda = 0.1 \text{ V}^{-1}$   
 $I_S = 10^{-15} \text{ A}$   
 $n = 1.13$

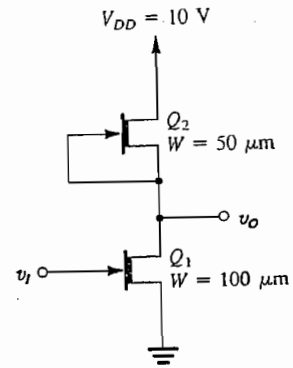


Fig. 4

5. For the op amp Schmitt trigger in Figure 5 determine the upper and lower trigger points as well as the hysteresis gap. Assume the positive and negative saturation levels of output voltage to be +11 and -11 V, respectively.

(20%)

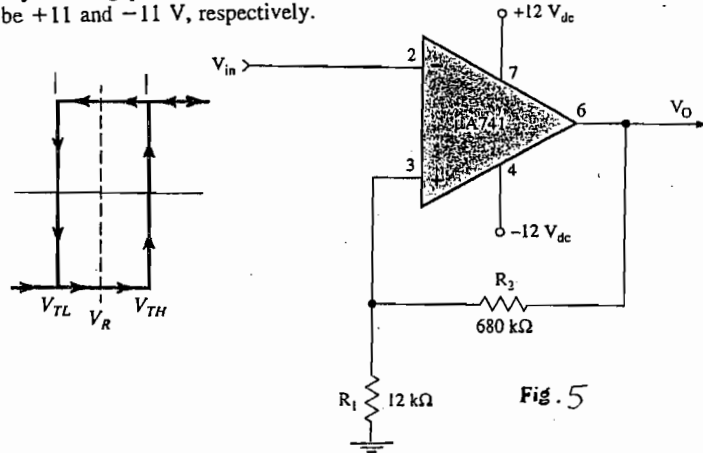


Fig. 5

6. Please explain circuit functions for Fig. 6 (10%)

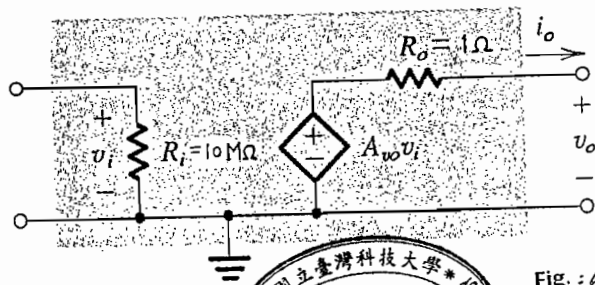


Fig. 6

90

