

國立台灣科技大學九十五學年度碩士班招生試題

系所組別：電機工程系碩士班乙二組、丙二組

科目：電子學

總分 100 分

1. Consider the circuit in Figure 1. Find the differential voltage gain

v_o / v_{id} . (10%)

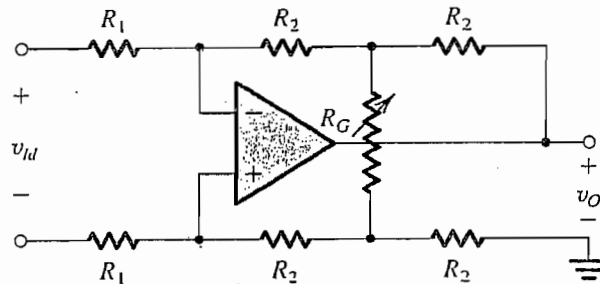


Figure 1

2. For the circuits in Figure 2, assume that each transistor is sized and biased so that $g_m = 1\text{mA/V}$ and $r_o = 100\text{k}\Omega$. Otherwise, ignore all dc biasing detail and concentrate on small-signal operation resulting in response to the input signal v_{sig} . For $R_L = 10\text{k}\Omega$, $R_1 = 500\text{k}\Omega$, and $R_2 = 1\text{M}\Omega$, find the overall voltage gain v_o / v_{sig} and the input resistance R_{in} for each circuit. (20%)

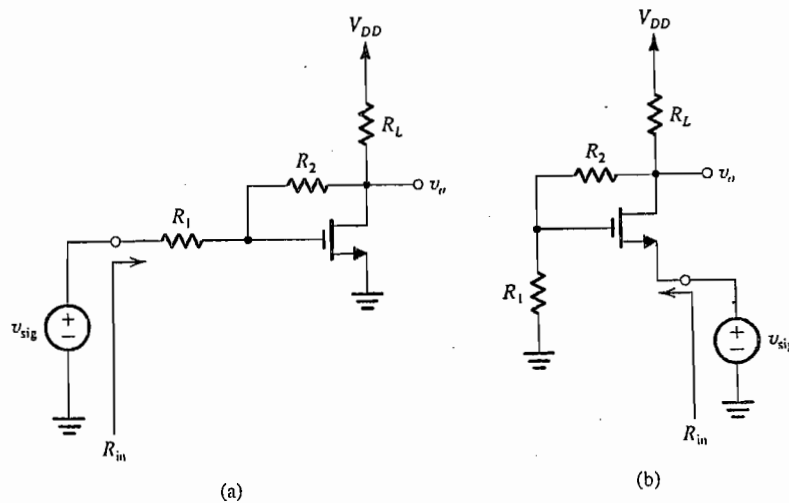


Figure 2



國立台灣科技大學九十五學年度碩士班招生試題

系所組別：電機工程系碩士班乙二組、丙二組

科 目：電子學

3. For the emitter follower shown in Figure 3, the signal source is directly coupled to the transistor base. If the dc component of v_{sig} is zero, find the dc emitter current. Assume $\beta = 100$ and $V_T = 25\text{mV}$. Neglecting r_o , finding R_{in} , the voltage gain v_o/v_{sig} , the current gain i_o/i_i , and the output resistance R_{out} . (20%)

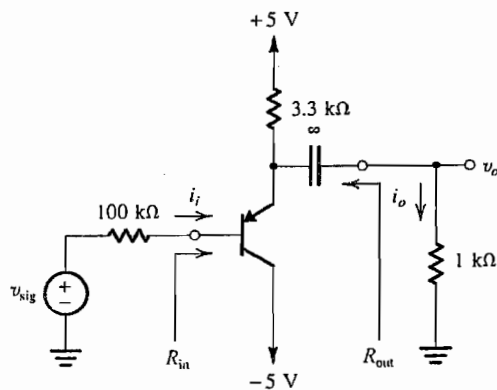


Figure 3

4. Find the quiescent values of I_C and V_{CE} in each of Q_1, Q_2, Q_3 , in Figure 4, assuming each transistor has $\beta=160$. (15%)

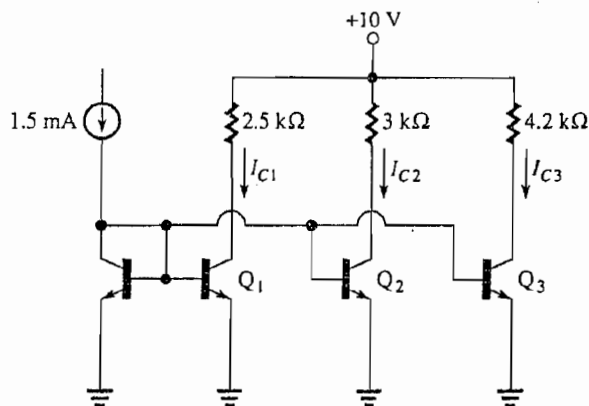


Figure 4



國立台灣科技大學九十五學年度碩士班招生試題

系所組別：電機工程系碩士班乙二組、丙二組

科 目：電子學

5. Let the op amp of Figure 5 have $r_d = 1 \text{ M}\Omega$, $a = 10^4 \text{ V/V}$, and $r_o = 100 \Omega$.

(a) Find β and loop gain, T . (10%)

(b) Find the ideal as well as the actual transfer characteristic of the circuit. (10%)

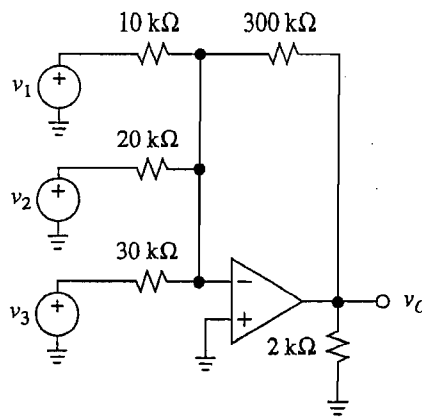


Figure 5

6. The gain of a certain amplifier as a function of frequency is

$$A(j\omega) = \frac{-16 \cdot 10^6}{j\omega}. \quad \text{A feedback path connected around it has}$$

$$\beta(j\omega) = \frac{10^3}{(2 \cdot 10^3 + j\omega)^2}. \quad \text{Will the system oscillate? If so, at what frequency? (15\%)}$$

