

國立台灣科技大學九十六學年度碩士班招生試題

系所組別：電機工程系碩士班乙二組、丙三組、乙二高職教師組

科 目：電子學

總分 100 分

1. Find the overall voltage gain, v_L/v_S , current gain, i_o/i_i , power gain, P_L/P_I , and discuss the function of each stage as shown in Fig. P1. (15 %)

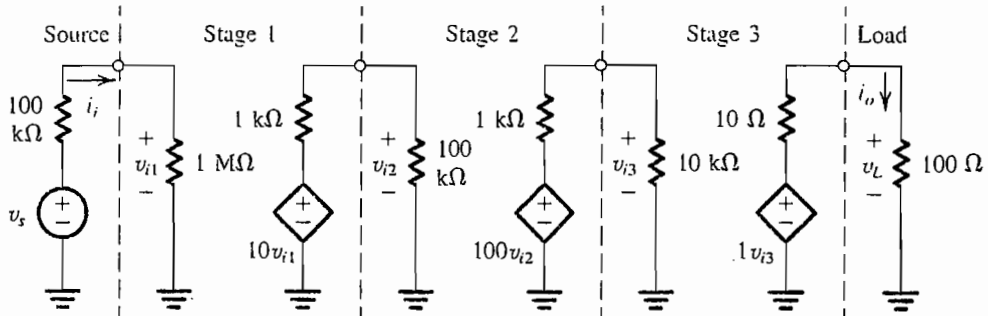


Fig. P1

2. (a) Assume the diodes to be ideal, find the value of **I** and **V** in the circuit of Fig. P2A. (5 %)

(b) Using exponential mode of the diode and iterative analysis to determine the current I_D and the diode voltage V_D for the circuit in Fig. P2B with $V_{DD}=5V$ and $R=1 k\Omega$. Assume that the diode has a current of 1 mA at the voltage of 0.7V and its voltage drop changes by 0.1V for every decade change in current. (10 %)

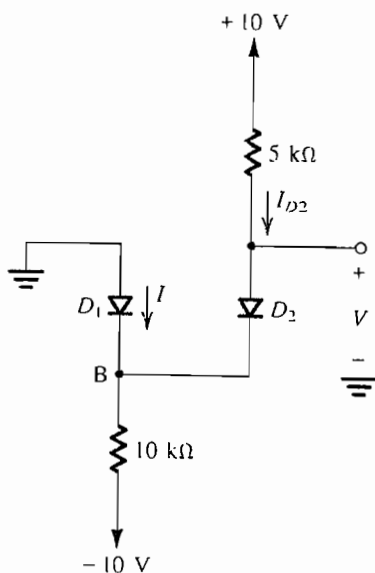


Fig. P2A

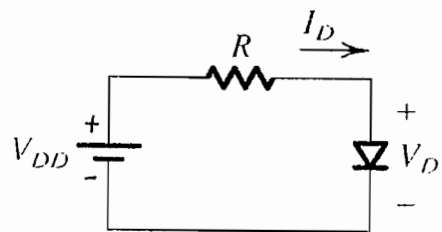


Fig. P2B

國立台灣科技大學九十六學年度碩士班招生試題

系所組別：電機工程系碩士班乙二組、丙三組、乙二高職教師組

科 目：電子學

3. (a) It is required to find the **midband gain** and **upper 3-dB frequency** f_H of the circuit as shown in Fig. P3 for the following case: (10 %)

$V_{CC} = V_{EE} = 10 \text{ V}$, $I = 1 \text{ mA}$, $R_B = 100 \text{ k}\Omega$, $R_C = 8 \text{ k}\Omega$, $R_{sig} = 5 \text{ k}\Omega$, $R_L = 5 \text{ k}\Omega$, $\beta_0 = 100$, $V_A = 100 \text{ V}$, $V_T = 25 \text{ mV}$, $C_\mu = 1 \text{ pF}$, $f_T = 800 \text{ MHz}$, and $r_x = 50 \Omega$.

- (b) Select appropriate values for C_{C1} , C_{C2} , and C_E to have lower 3-dB frequency $f_L = 120 \text{ Hz}$. Let the values of C_{C1} , C_{C2} , and C_E are selected to contribute 0.1, 0.1, and 0.8 of the value of ω_L . (10 %)

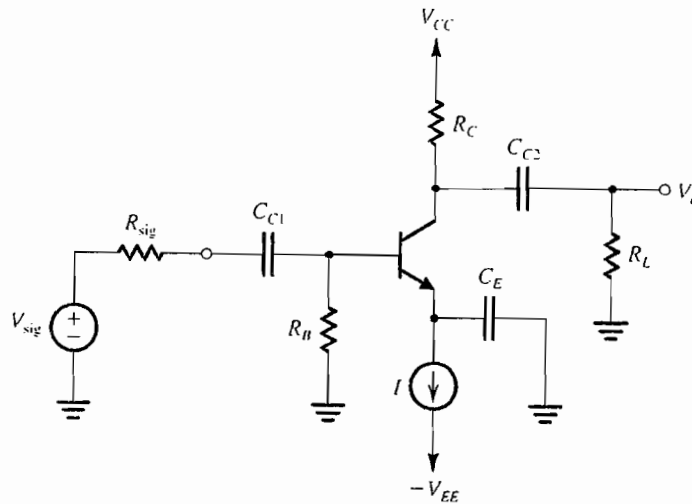


Fig. P3

國立台灣科技大學九十六學年度碩士班招生試題

系所組別： 電機工程系碩士班乙二組、丙三組、乙二高職教師組

科 目： 電子學

4. For the circuit shown in Fig. P4, assume that both OPAs are ideal and $V_{REF} = 1V$.
- Explain why the currents flow through both R_1 are equal even $\delta \neq 0$. (5%)
 - Denote the output of OA_1 as v_{o1} . Derive the relationship between v_{o1} and δ . (8%)
 - Derive the relationship between v_o and δ . (8%)

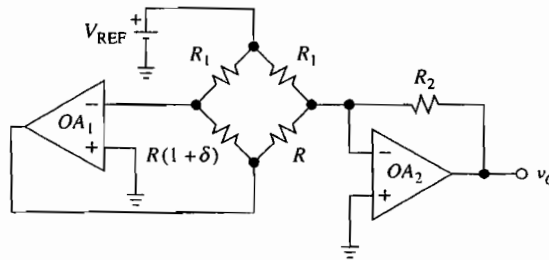


Fig. P4

5. The OPA in the circuit of Fig. P5 has an open-loop transfer function

$$A(s) = \frac{10^5}{1 + s/20}$$

- Derive the transfer function of the loop gain $A(s)\beta(s)$. (5%)
- By asymptotic approach, sketch the magnitude of the loop gain in dB versus frequency on a logarithmic scale. [Hint: $\log 20 = 1.301$] (6%)
- Find the frequency at which $|A(j\omega)\beta(j\omega)| = 1$. (6%)

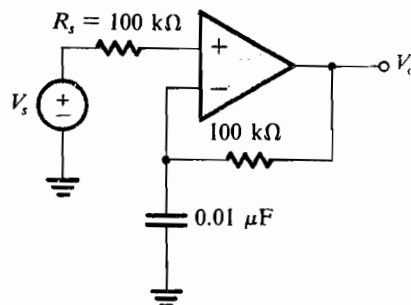


Fig. P5

國立台灣科技大學九十六學年度碩士班招生試題

系所組別：電機工程系碩士班乙二組、丙三組、乙二高職教師組

科 目：電子學

6. The circuit of Fig. P6 is a band-pass filter. Assume that the OPA is ideal and the values of the components are as follow: $R_1 = R_2 = 10\text{k}\Omega$ and $C_1 = C_2 = 0.1\mu\text{F}$.
- (a) Derive the transfer function of this band-pass filter. (6%)
- (b) Calculate the center frequency and Q factor of this filter. (6%)

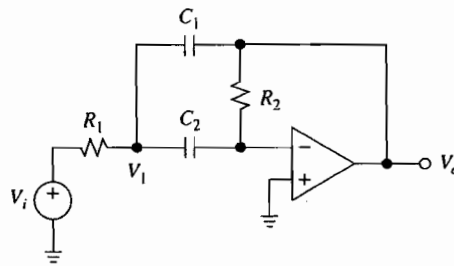


Fig. P6