

國立台灣科技大學九十九學年度碩士班招生試題

系所組別： 電子工程系碩士班乙二組

科 目： 電子學

(總分為100分)

- For the circuit shown in Fig. 1, the BJT parameters are $V_A=\infty$, $V_{BE(on)}=0.7\text{ V}$, $\beta=100$, and $V_T=26\text{ mV}$. (a) (5%) Calculate the dc current I_B and I_C . (b) (5%) Draw the small-signal equivalent circuit of this circuit. (c) (5%) Find the small-signal voltage gain $A_v=v_{out}/v_{in}$. (d) (5%) Determine the small-signal input resistance r_{in} and the output resistance r_{out} .

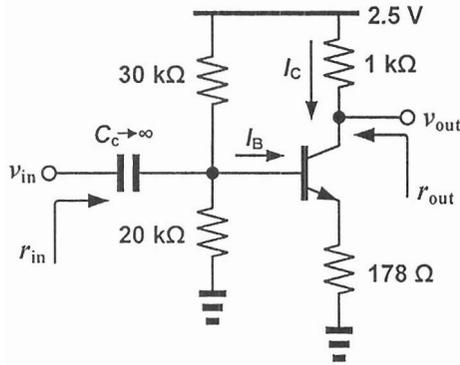


Fig. 1

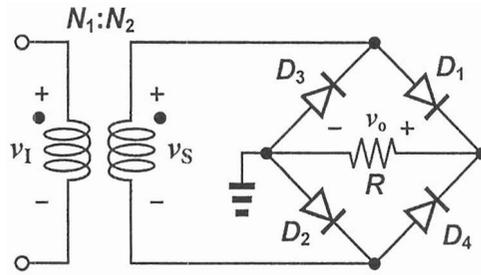


Fig. 2

- The full-wave rectifier shown in Fig. 2 has a load resistor $R=150\ \Omega$. Assume the input voltage is from a 120 V_{rms} , 60 Hz ac source, the diode cut-in voltage is 0.7 V , and the desired output peak voltage v_o is 12 V . (a) (3%) Please find out the turns ratio N_1/N_2 of the transformer. (b) (3%) What is the peak inverse voltage (PIV) of each diode? (c) (4%) If the ripple voltage is to be smaller than 0.3 V , determine the required value of the filter capacitor in parallel with R .
- For the circuit shown in Fig. 3, the NMOS transistors parameters are $V_{TN1}=V_{TN2}=0.5\text{ V}$, $K_{n1}=K_{n2}=1\text{ mA/V}^2$, and $\lambda=0$. The resistors values are $R_1=10\text{ k}\Omega$, $R_{S1}=500\ \Omega$. (a) (9%) Determine R_2 , R_{D1} , and R_{S2} such that $I_{D1}=I_{D2}=1\text{ mA}$, and $V_{DS2}=2.5\text{ V}$. (b) (5%) Find the small-signal voltage gain $A_v=v_{out}/v_{in}$. (c) (6%) Find the small-signal input resistance r_{in} and the output resistance r_{out} .

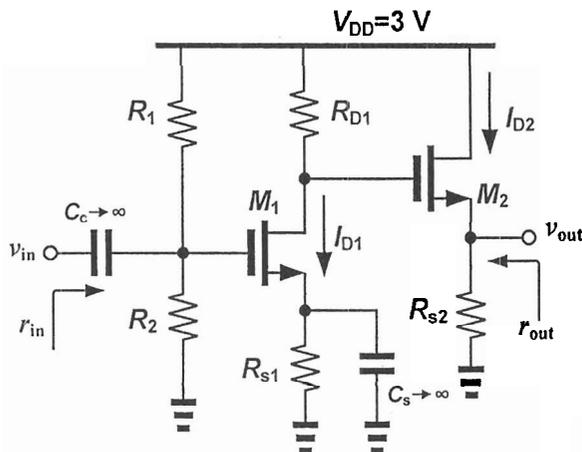


Fig. 3



國立台灣科技大學九十九學年度碩士班招生試題

系所組別：電子工程系碩士班乙二組

科目：電子學

(總分為100分)

4. (8%) Determine the voltage gain $A_v = v_o / v_i$ for the ideal operational amplifier circuit in Fig. 4.

5. For the MOSFET differential amplifier circuit shown in Fig. 5. The transistor parameters are:

$K_{n1} = K_{n2} = 0.1 \text{ mA/V}^2$, $K_{n3} = K_{n4} = 0.2 \text{ mA/V}^2$, $\lambda = 0.01$ and $V_{TN} = 1 \text{ V}$ for all transistors,

and $R_D = 15 \text{ k}\Omega$, $R_1 = 30 \text{ k}\Omega$. (a) (5%) Calculate the dc current I_1 , I_Q , and I_{D1} . (b) (7%)

Determine the differential-mode voltage gain $A_d = v_{O2} / v_d$, where $v_d = v_1 - v_2$. (c) (7%)

Determine the common-mode voltage gain $A_{cm} = v_{O2} / v_{cm}$, where $v_{cm} = (v_1 + v_2) / 2$. (d) (5%)

Find the CMRR for this differential amplifier.

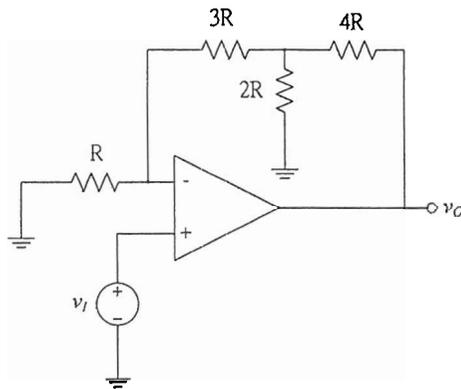


Figure 4

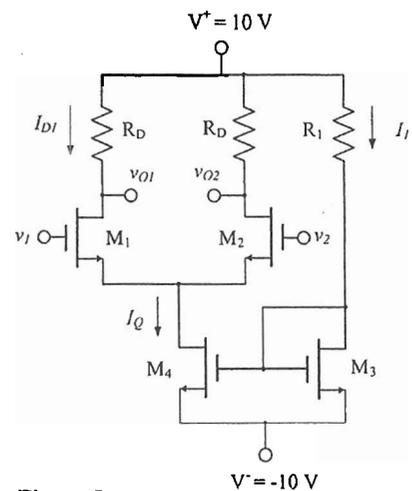


Figure 5

6. For the circuit in Fig. 6, $R_1 = 10 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$. The open-loop operational amplifier parameters are: input resistance $R_i = 60 \text{ k}\Omega$, voltage gain $A_v = 10000$. (a) (6%) Determine the feedback transfer function β . (b) (6%) Determine the close-loop gain A_{vf} . (c) (6%) Determine the close-loop input resistance R_{if} .

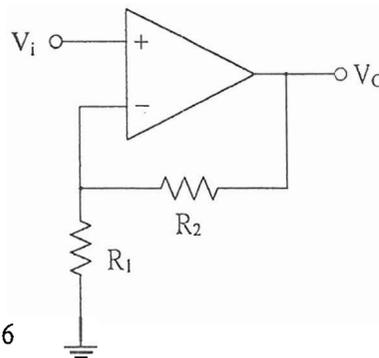


Figure 6

